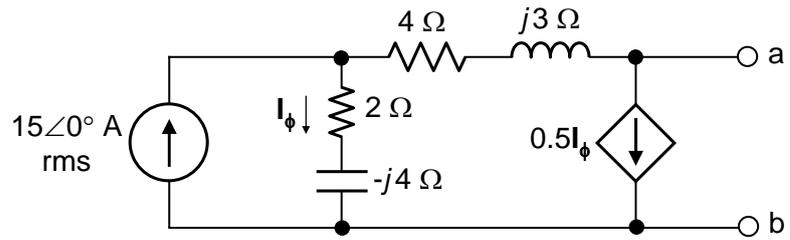


**Problem (12 pts)**

Consider the circuit shown



- a. Determine the open-circuit voltage at terminals a and b. (3 pts)

$$15 = 1.5I_\phi; I_\phi = 10 \text{ A}; V_{Th} = 10(2 - j4) - 5(4 - j3) = -j55 \text{ V.}$$

- b. Determine the current flowing in the short circuit when there is a short between terminals a and b. (3 pts)

$15 = 1.5I_\phi + I_{sc};$   
 $I_\phi(2 - j4) = (0.5I_\phi + I_{sc})(4 + j3);$   
 solving these two equations gives  
 $I_{sc} = \frac{165}{74}(1 - j6) \text{ A}$

- c. Determine the equivalent impedance  $Z_{Th}$  as seen by the terminals a and b. (2 pts)

$$Z_{Th} = |V_{Th}|/|I_{sc}| = \frac{j55 \times 74}{165(1 - j6)} = 4 - j\frac{2}{3} \Omega$$

- d. Evaluate  $Z_{Th}$  again using a different method than that employed in part (c). (4 pts)

$I_T = 1.5I_\phi; V_T = I_\phi(6 - j)$   
 dividing gives:  
 $Z_{Th} = \frac{6 - j}{1.5} = 4 - j\frac{2}{3} \Omega.$


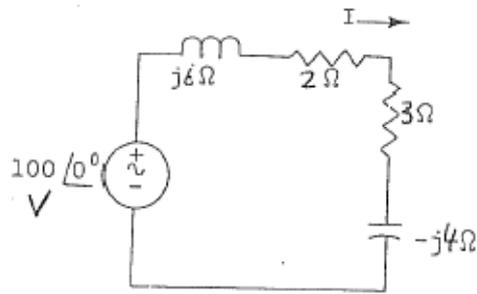


Figure 4.

4. Find the current in the circuit shown in figure 4.

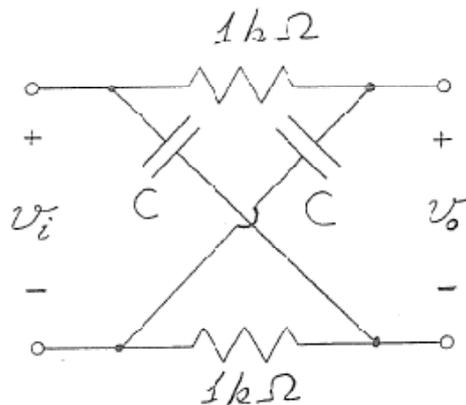- A.  $18.6 \angle -21.8^\circ$  A
- B.  $22.5 \angle -35.6^\circ$  A
- C.  $12.3 \angle -18.9^\circ$  A
- D.  $34.7 \angle -29.7^\circ$  A
- E. None of the above



Hint: redraw lattice circuit as a bridge

Figure 9.

9. Determine  $C$  in the circuit shown in figure 9 so that the output voltage  $v_o$  has the same magnitude as the input voltage  $v_i$  but lags it by  $90^\circ$ , assuming  $\omega = 200$  rad/s.

- A.  $5 \mu\text{F}$
- B.  $2 \mu\text{F}$
- C.  $6 \mu\text{F}$
- D.  $8 \mu\text{F}$
- E. None of the above

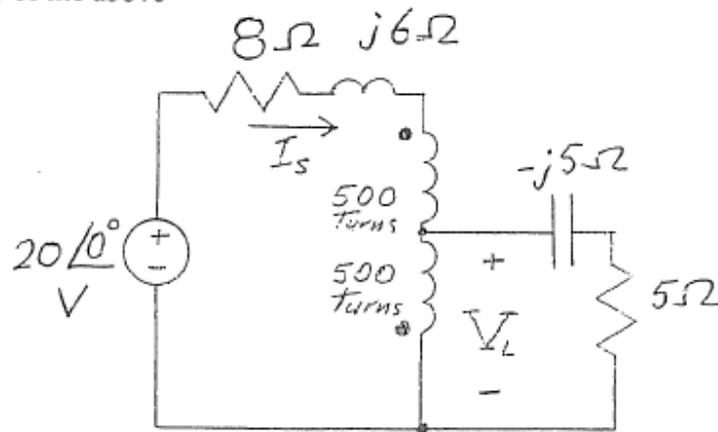


Figure 12.

12. Determine  $I_s$  and  $V_L$  in the circuit shown in figure 12.


- A.  $1.4 \angle -45.0^\circ$  A, 0 V
- B.  $0.7 \angle -45.0^\circ$  A,  $0.3 \angle 45.0^\circ$  V
- C.  $1.4 \angle -36.3^\circ$  A,  $0.3 \angle 14.4^\circ$  V
- D.  $1.1 \angle -45.0^\circ$  A,  $0.4 \angle 45.0^\circ$  V
- E. None of the above

Hint: determine current in  $(5 - j5)$  ohms, assuming autotransformer is ideal

$2 \angle -36.9^\circ$  A, 0 V

4. Find the expression of  $v_L(t)$  in the circuit shown in Fig. 3.

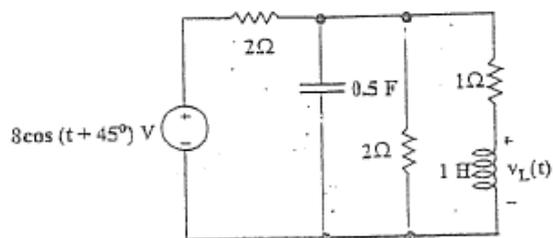- A.  $v_L(t) = 1.89 \cos(t + 90^\circ)$  V
- B.  $v_L(t) = 1.24 \cos(t - 90^\circ)$  V
- C.  $v_L(t) = 2.58 \cos(t + 45^\circ)$  V
- D.  $v_L(t) = 0.96 \cos(t - 45^\circ)$  V
- E. None of the above



6. Find  $v_o$  in the circuit shown in Fig. 5 if  $\omega = 5 \times 10^6$  rad/s.

- A.  $14.7 / 21.8^\circ$  V  
 B.  $11.6 / 15.6^\circ$  V  
 C.  $12.8 / 35.2^\circ$  V  
 D.  $10.5 / 25.9^\circ$  V

→ E. None of the above **10.5 @ 19.8 deg**


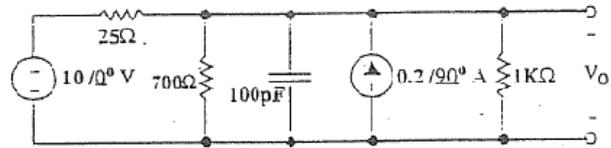


Figure 5.

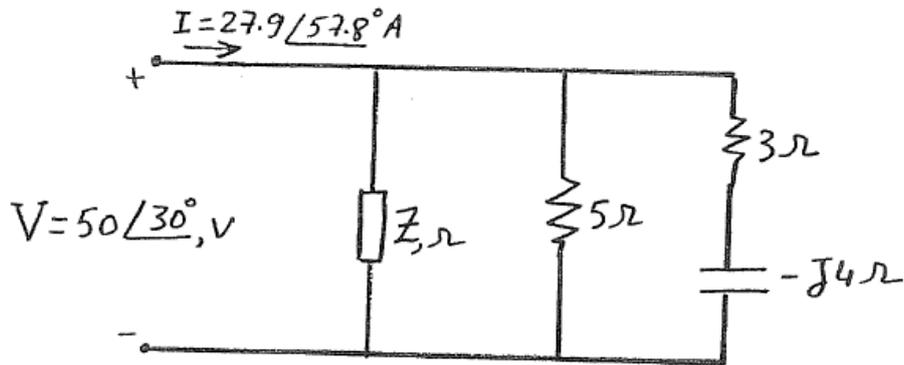
12. Determine  $Z$  in the circuit shown below:




- A.  $0.2 < 29.9^\circ \Omega$   
 B.  $5 \Omega$   
 → C.  $5 < -29.9^\circ \Omega$   
 D.  $1.8 < -27.8^\circ \Omega$   
 E. None of the above.

3. In the circuit shown,  $V_{AB} = 48.3 < 30^\circ$  V. Find  $V_{in}$

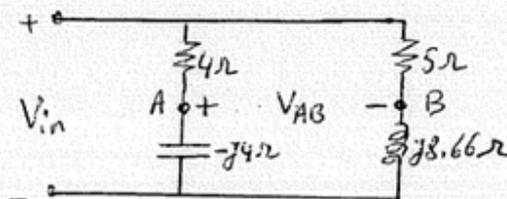- a.  $50 < 135^\circ$  V  
 b.  $36 < 45^\circ$  V  
 c.  $80 < 135^\circ$  V  
 d.  $73 < 45^\circ$  V  
 e. None of the above



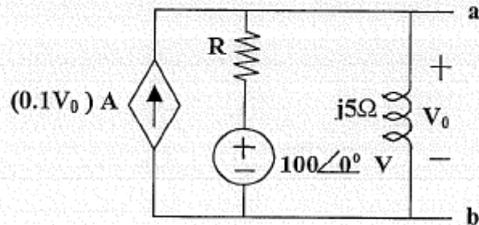11. Considering the circuit below find its Thevenin impedance between a and b.




$R = 2\Omega$

- a)  $(2 + j1)\Omega$
- b)  $(2 + j4)\Omega$
- c)  $(j5)\Omega$
- d)  $(j2)\Omega$
- e. None of the above


19. Determine Thevenin's impedance looking into terminals ab, given the reactance of  $C$  is  $-j 10 \Omega$ .

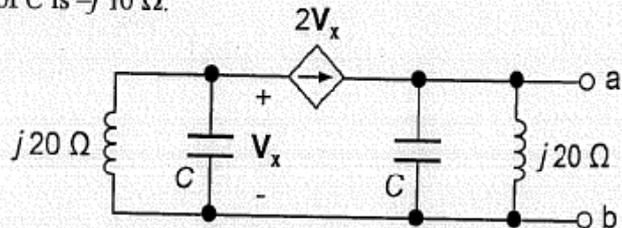- A.  $-j 20 \Omega$
- B.  $+j 20 \Omega$
- C.  $-j 40 \Omega$
- D.  $+j 40 \Omega$
- E. None of the above



8%

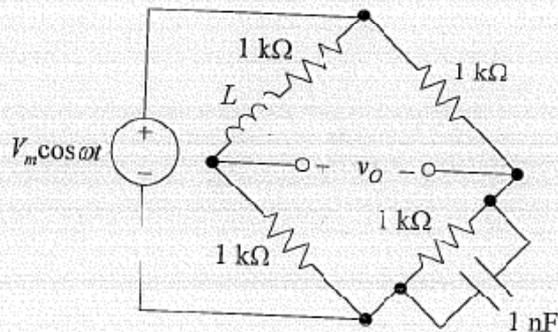6. Determine  $L$  so that the bridge is balanced ( $v_o = 0$ ) at  $\omega = 10^6$  rad/s.
- A. 1 mH                      B. 2  $\mu$ H  
C. 4  $\mu$ H                      D. 1 H  
E. None of the above




**Solution:** At balance,  $\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$ ;

$$Z_2 = \frac{R / j\omega C}{R + 1 / j\omega C} = \frac{R}{1 + j\omega CR}; \Omega.$$

$$\frac{Z_1}{Z_2} = 1 + j\omega CR. \text{ Hence, } \frac{R + j\omega L}{R} =$$

$$1 + \frac{j\omega L}{R} = 1 + j\omega CR, \text{ or}$$

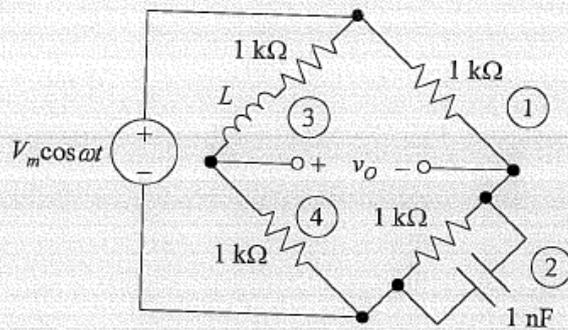
$$L = CR^2 = 10^{-9} \times 10^6 = 1 \text{ mH.}$$



7%

5. Determine  $I_L$ , given that  $\omega = 100$  rad/s.

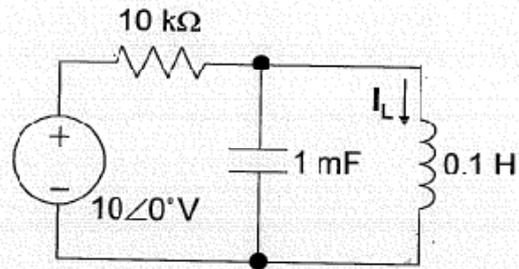
- A. zero
- B. infinite
- C.  $1\angle 90^\circ$  A
- D.  $1\angle -90^\circ$  A
- E. None of the above



8%

2. Determine  $I_C$ , given that  $\omega = 2$  krad/s

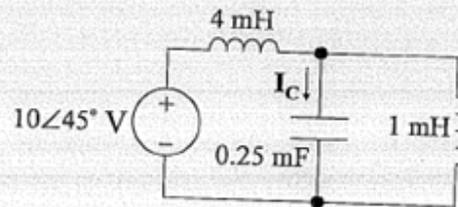- A.  $5\angle 135^\circ$  A
- B.  $10\angle 45^\circ$  A
- C.  $5\angle -45^\circ$  A
- D.  $10\angle 90^\circ$
- E. None of the above




**Solution:**  $j\omega L = j2 \times 10^3 \times 10^{-3} = j2\ \Omega$ ;  $\frac{1}{j\omega C} = \frac{1}{j2 \times 10^3 \times 0.25 \times 10^{-3}} = -j2\ \Omega$ .

The parallel impedance of  $j2\ \Omega$  and  $-j2\ \Omega$  is infinite, so that no current flows in the  $4\text{ mH}$


inductor. The voltage across the capacitor is  $10\angle 45^\circ$  V, and  $I_C = \frac{10\angle 45^\circ}{-j2} = 5\angle 135^\circ$  A.

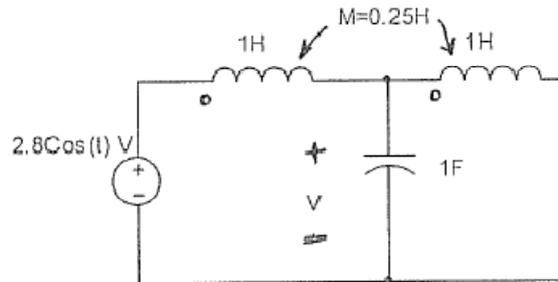-7- Find the voltage across the capacitor of the circuit shown.



- a.  $\text{Cos}(2.26t)$    b. 0   c.  $2.26\text{Cos}(t)$    d.  $0.25\text{Cos}(t)$   
 f. None of the above

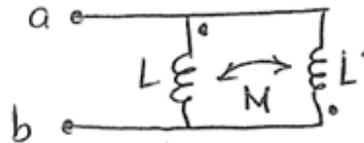7. Find the equivalent inductance for the following connection, such that:  $L=60\text{mH}$ ,  $L'=80\text{mH}$  and  $M=100\text{mH}$ .



- a)  $34.2\text{mH}$    b)  $86.6\text{mH}$    c)  $-15.3\text{mH}$    d)  $134.2\text{mH}$    e) NOA

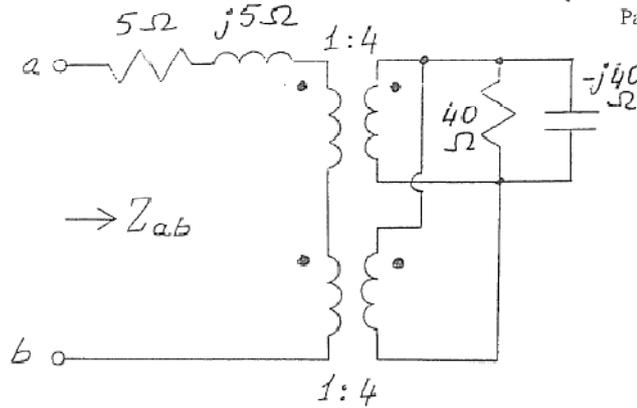


Figure 7.

7. Two identical transformers are connected as shown in figure 7. Determine the impedance  $Z_{ab}$ .

- A.  $10 \Omega$
- B.  $15 \Omega$
- C.  $10 + j10 \Omega$
- D.  $10 - j10 \Omega$
- E. None of the above

3. Calculate the voltages  $v_1$  and  $v_2$  in the circuit of Fig. 2.

- A.  $v_1 = -10 \cos t \text{ V}; v_2 = -9 \cos t \text{ V}$
- B.  $v_1 = 10 \cos t \text{ V}; v_2 = 9 \cos t \text{ V}$
- C.  $v_1 = 10 \cos t \text{ V}; v_2 = -9 \cos t \text{ V}$
- D.  $v_1 = 9 \cos t \text{ V}; v_2 = -10 \cos t \text{ V}$
- E. None of the above

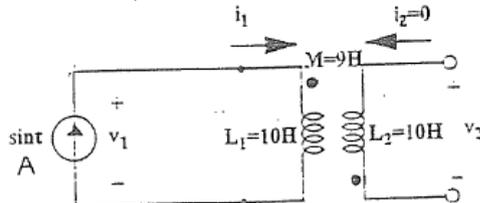


Figure 2.

8. Find the turns ratio for the ideal transformer shown in Fig. 7 required to match the 200 ohms source impedance to the 8 ohms load.

- A.  $n = 3$
- B.  $n = 4$
- C.  $n = 5$
- D.  $n = 6$
- E. None of the above

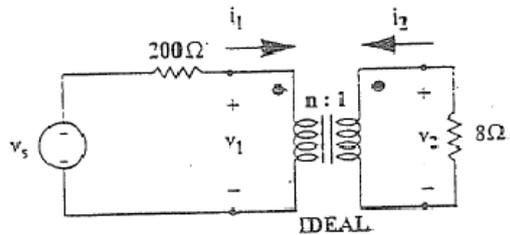


Figure 7.

15. Determine the Thevenin equivalent circuit between terminals  $a$  and  $b$  in Fig. 13 if  $V_s = 10 \angle 0^\circ$  V.

- A.  $V_{Th} = 40$  V;  $R_{Th} = 25 \Omega$   
 B.  $V_{Th} = 20$  V;  $R_{Th} = 25 \Omega$   
 C.  $V_{Th} = 40$  V;  $R_{Th} = 50 \Omega$   
 D.  $V_{Th} = 20$  V;  $R_{Th} = 50 \Omega$   
 E. None of the above

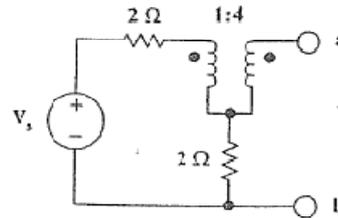


Figure 13

19. Determine  $L_{eq}$  in Fig. 16 if  $L_3 = 1 \mu\text{H}$ .

- A.  $8 \mu\text{H}$   
 B.  $6 \mu\text{H}$   
 C.  $4 \mu\text{H}$   
 D.  $3 \mu\text{H}$   
 E. None of the above

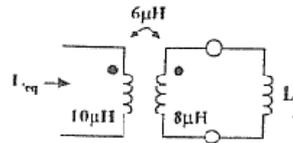


Figure 16

20. If  $I_1 = 2$  A in Fig. 17, find the value of  $I_2$  that will minimize the stored energy.

- A. 1.33 A  
 B. 2 A  
 C. 0  
 D. 0.67 A  
 E. None of the above


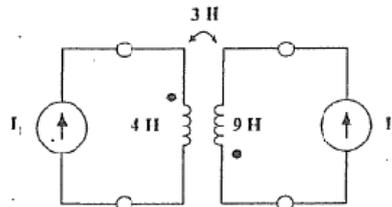



Figure 17

2. Find the input impedance  $Z_{AB}$  in the circuit shown below.

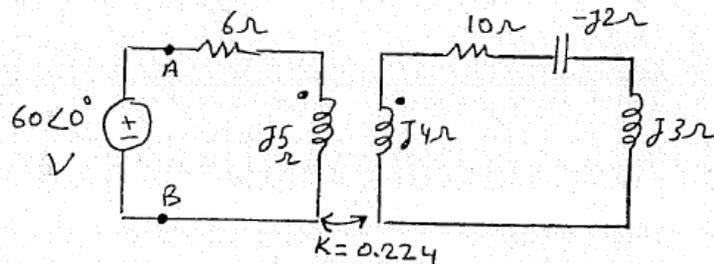- A.  $6 + j5.896 \Omega$   
 B.  $8.3 + j4.7 \Omega$   
 C.  $6.1 + j5 \Omega$   
 D.  $3.8 + j9.2 \Omega$   
 E. None of the above




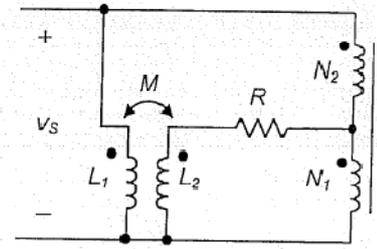5. In the figure shown,  $v_s = 10\cos 100\pi t$  V,  $L_1 = 120$  mH,  $L_2 = 30$  mH,  $R = 100$  ohms,  $N_1 = 400$  turns, and  $N_2 = 1600$  turns. Determine the coupling coefficient so that no current flows in the 100 ohm resistor.



- A. 0.4  
 B. 0.5  
 C. 0.6  
 D. 0.8  
 E. None of the above

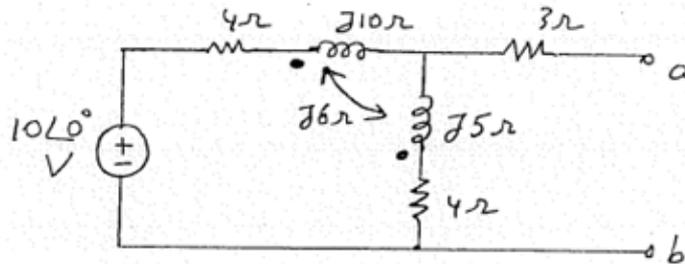9. In the circuit shown below, find the Thevenin equivalent circuit as seen from terminals a-b.



- A.  $V_{Thev} = 4.82 \angle -34.60^\circ$  V,  $Z_{Thev} = 8.62 \angle 48.79^\circ \Omega$   
 B.  $V_{Thev} = 4.82 \angle 34.60^\circ$  V,  $Z_{Thev} = 8.62 \angle 40.38^\circ \Omega$   
 C.  $V_{Thev} = 48.2 \angle -34.60^\circ$  V,  $Z_{Thev} = 86.2 \angle 48.79^\circ \Omega$   
 D.  $V_{Thev} = 5 \angle -34.60^\circ$  V,  $Z_{Thev} = 8.1 \angle 48.79^\circ \Omega$   
 E. None of the above

12. Consider a source  $V_s$  supplying the primary of a transformer. The secondary is connected to a purely capacitive load  $Z_c$ . The primary impedance is  $Z_1$ , the secondary impedance is  $Z_2$ , and the mutual impedance between primary and secondary is  $Z_m$ . Calculate the currents  $I_1$  at primary and  $I_2$  at secondary.

Given:  $V_s = 150 \angle 0^\circ$  V,  $Z_1 = j3600 \Omega$ ,  $Z_2 = j2500 \Omega$ ,  $Z_m = j1200 \Omega$ ,  $Z_c = -j2400$

- A.  $I_1 = 13.9 \angle -90^\circ$  mA,  $I_2 = 166.6 \angle +90^\circ$  mA  
 B.  $I_1 = 13.9 \angle 0^\circ$  mA,  $I_2 = 166.6 \angle +180^\circ$  mA  
 C.  $I_1 = 33.5 \angle -90^\circ$  mA,  $I_2 = 356.5 \angle +90^\circ$  mA  
 D.  $I_1 = 33.5 \angle 0^\circ$  mA,  $I_2 = 356.5 \angle +180^\circ$  mA  
 E. None of the above


Assume dot markings are both up

1. Two magnetically coupled coils have a coefficient of coupling  $K=0.5$ . When they are connected in series, their total inductance is 80 mH. When connection of one of the coils is reversed, the total inductance becomes 40 mH. Specify which of the following represents the self-inductance of one of the coils  $L$ .


- A. 60 mH
- B. 52.36 mH
- C. 40 mH
- D. 5.64 mH
- E. None of the above

8. Determine  $I$ .

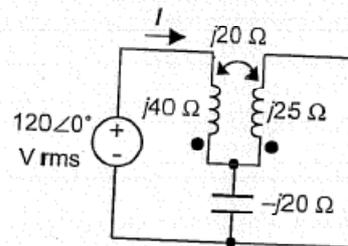- A.  $+j4$  A rms
- B.  $-j6$  A rms
- C.  $-j4.8$  A rms
- D.  $-j8$  A rms
- E. None of the above




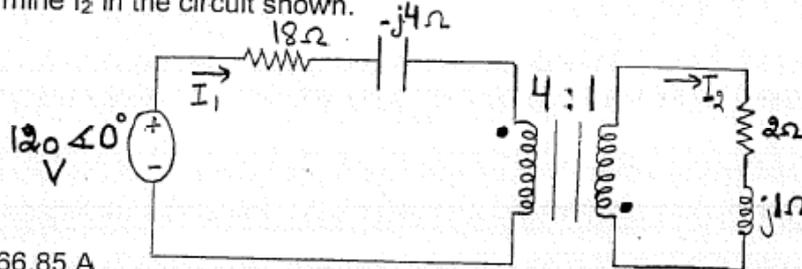11. Determine  $I_2$  in the circuit shown.



- A.  $25.61 \angle 166.85^\circ$  A
- B.  $3.56 \angle -166.85^\circ$  A
- C.  $16.42 \angle -13.15^\circ$  A
- D.  $9.33 \angle -193.15^\circ$  A
- E. None of the above

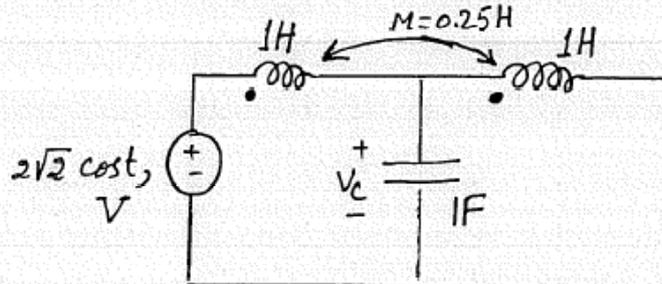
5. Find the voltage  $V_c(t)$  across the capacitor of the circuit shown below.



- a.  $1.6 \cos t$ , V
- b.  $1.41 \cos t$ , V
- c.  $2.26 \cos t$ , V
- d.  $\cos t$ , V
- e. None of the above


3. Determine the total energy stored in the capacitors and inductors after the switch has been closed for a long time, assuming  $V_s = 8$  V.

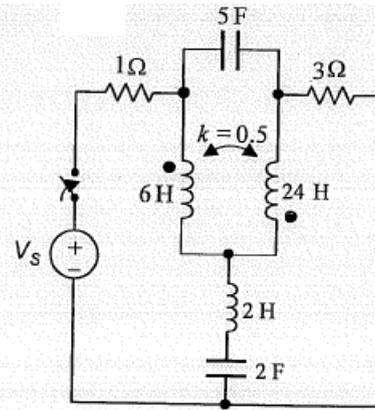- A. 12 J  
 B. 30 J  
 → C. 120 J  
 D. 148 J  
 E. None of the above




- 7%  
 4. If the dot marking on one of the coils is reversed, the damping coefficient  $\alpha$

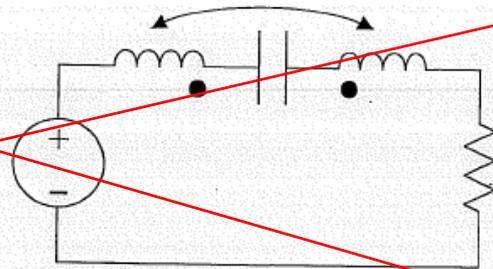- A. increases  
 — B. decreases  
 C. remains the same



- 7%  
 7. Determine the minimum value of  $Z_{in}$  as  $R_L$  is varied between zero and infinity.

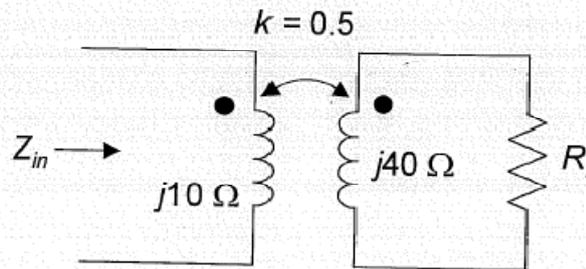- A.  $j5 \Omega$   
 — B.  $j7.5 \Omega$   
 C.  $j10 \Omega$   
 D. 0  
 E. None of the above




17%

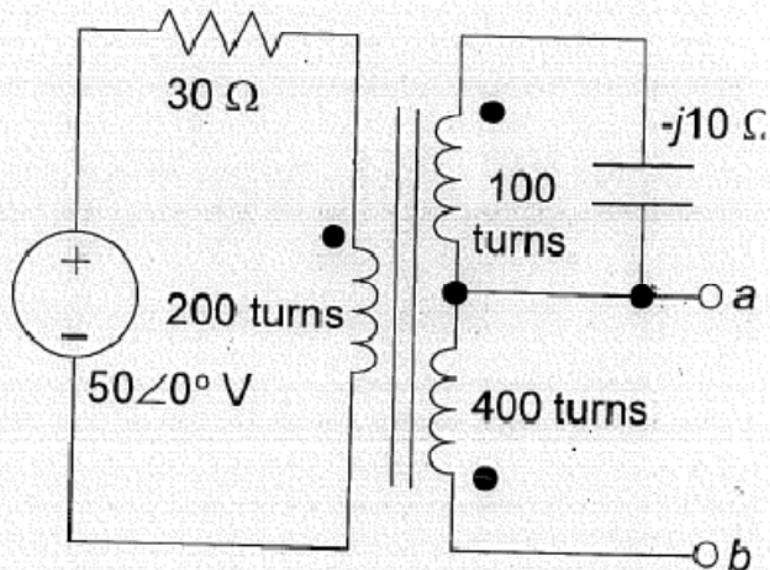9. Determine Thevenin's equivalent circuit between terminals ab, assuming the transformer is ideal.

$$V_{Th} = -64 + j48 \text{ V}$$

$$Z_{Th} = \frac{96}{5} (4 - j3) \Omega$$



The sinusoidal current source  $i(t)$  is given by:


$$i(t) = 10 \sin(120\pi t) \text{ (Amps)}$$


$$t \geq 0$$

This current is applied to the primary coil of a transformer, as shown below. The primary coil (self-inductance 2H) is 100%-coupled to the secondary coil (self-inductance 4.5H).

Find the value of the voltage  $v_o$ , at  $t = 0$ .

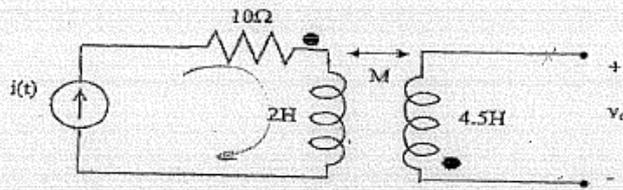
- (a) 15.75 kV
- (b) -11.31 kV
- (c) -15.75 kV
- (d) 11.31 kV
- (e) None of these



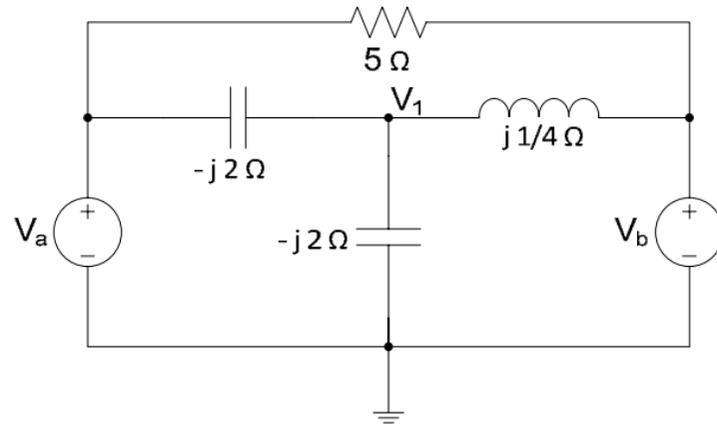


1. Find the correct node-equation for the voltage  $V_1$ .

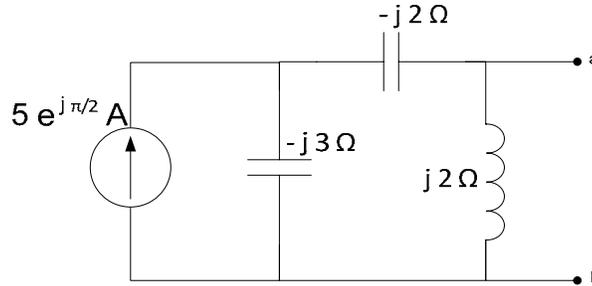- a)  $6V_1 + V_a - 8V_b = 0$
- b)  $2V_1 + V_a - 4V_b = 0$
- c)  $V_1 - V_a + V_b = 0$
- d)  $3V_1 - 2V_a + V_b = 0$
- e)  $7V_1 - 4V_a + V_b = 0$



4. Find the Thevenin equivalent circuit with respect to the terminals a-b. What are the values of  $V_{Th}$  in V and  $Z_{Th}$  in  $\Omega$ ?

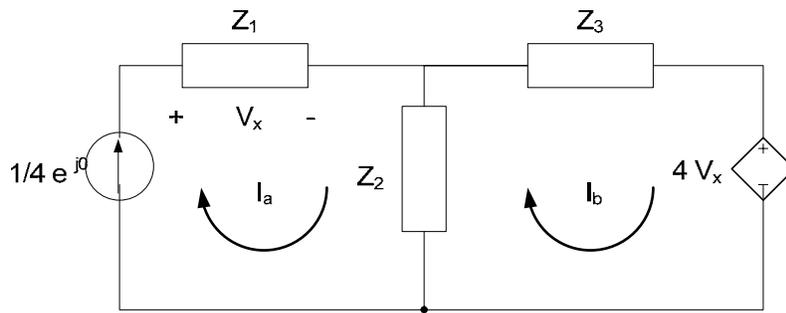- a)  $V_{Th} = -10 \text{ V}$ ,  $Z_{Th} = j10/3 \Omega$
- b)  $V_{Th} = -8 \text{ V}$ ,  $Z_{Th} = j3 \Omega$
- c)  $V_{Th} = -6 \text{ V}$ ,  $Z_{Th} = j14/5 \Omega$
- d)  $V_{Th} = -4 \text{ V}$ ,  $Z_{Th} = j8/3 \Omega$
- e)  $V_{Th} = -2 \text{ V}$ ,  $Z_{Th} = j5/2 \Omega$



5. What is the expression for  $V_x$ ?

- a)  $(Z_1 + Z_2)$
- b)  $5 Z_1$
- c)  $Z_1/4$
- d)  $2 Z_1$
- e)  $Z_1/2$

6. What is the correct set of equations for the mesh currents  $I_a$  and  $I_b$ ?

- a)  $I_a(-Z_1 + 4Z_2) - I_b(4Z_2 + 4Z_3) = 0, I_a - 5 = 0$
- b)  $I_a(-Z_1 + 2Z_2) - I_b(2Z_2 + 2Z_3) = 0, I_a - 2 = 0$
- c)  $I_a(-Z_1 + Z_2) - I_b(Z_2 + Z_3) = 0, I_a - 1 = 0$
- d)  $I_a(-2Z_1 + Z_2) - I_b(Z_2 + Z_3) = 0, I_a - 1/2 = 0$
- e)  $I_a(-4Z_1 + Z_2) - I_b(Z_2 + Z_3) = 0, I_a - 1/4 = 0$


17. If a capacitor with impedance  $Z_2$  is connected in parallel to a load  $Z_1 = 300 + j450 \Omega$ . What should be  $Z_2$  in ohms so that the equivalent load is purely resistive?

- a)  $-928.6 j$
- b)  $-1112.5 j$
-  c)  $-650 j$
- d)  $-750 j$
- e) None of the above

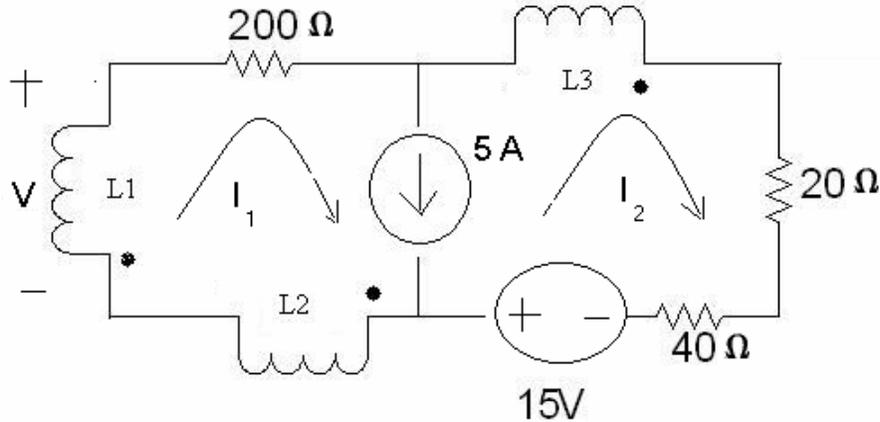22. Assuming that the voltage  $V$  across inductance  $L1$  is as shown in figure below and that the mutual inductance between


- $L1$  and  $L2$  is  $M12$
- $L1$  and  $L3$  is  $M13$
- $L2$  and  $L3$  is  $M23$

Use the mesh technique to find the expression of the voltage  $V$ .



- a)  $V = -L_1 \frac{dI_1}{dt} - M_{12} \frac{dI_1}{dt} + M_{13} \frac{dI_2}{dt}$   
 b)  $V = -L_1 \frac{dI_1}{dt} + M_{12} \frac{dI_1}{dt} + M_{13} \frac{dI_2}{dt}$   
 c)  $V = -L_1 \frac{dI_1}{dt} + M_{12} \frac{dI_1}{dt} - M_{13} \frac{dI_2}{dt}$   
 d)  $V = -L_1 \frac{dI_1}{dt} + M_{12} \frac{dI_1}{dt} + M_{13} \frac{dI_2}{dt}$   
 e) None of the above

**Problem 1**

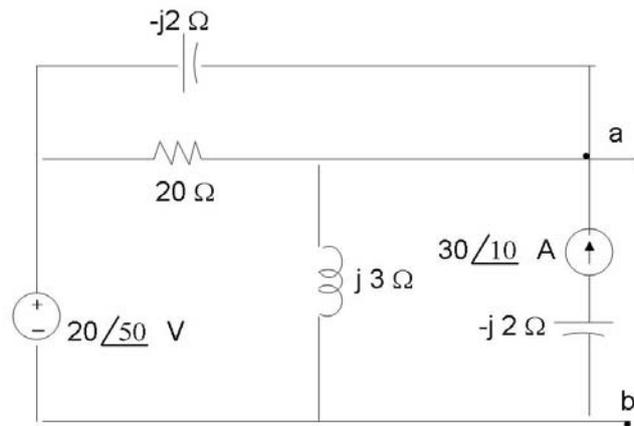


Find  $Z_{th}$  across a and b

- A)  $Z_{th} = 3.85 - j 0.77 \Omega$
- B)  $Z_{th} = 1.65 - j 5.50 \Omega$
- C)  $Z_{th} = 5.29 - j 8.82 \Omega$
- D)  $Z_{th} = 6.50 - j 1.65 \Omega$
- E) None of the above

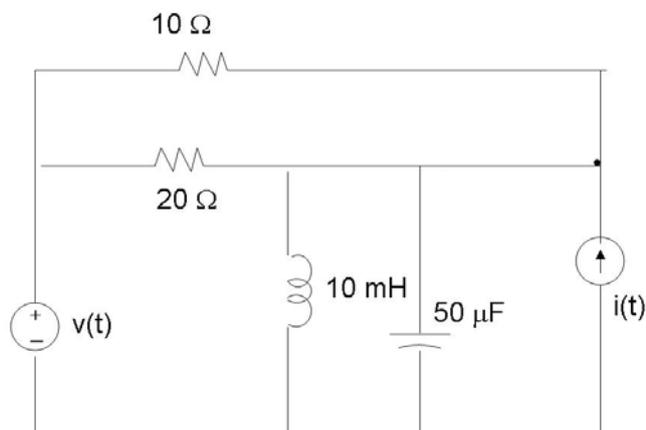**Problem 2**


What are the impedances in this circuit if  $v(t) = 20 \cos(10t + 50^\circ)$  Volts and  $i(t) = 50 \cos(10t + 20^\circ)$  Amperes.



- A)  $10 \Omega, 20 \Omega, -j 0.1 \Omega, j 0.05 \Omega$
- B)  $10 \Omega, 20 \Omega, -j 1.0 \Omega, j 0.05 \Omega$
- C)  $10 \Omega, 20 \Omega, j 0.1 \Omega, -j 2000 \Omega$
- D)  $10 \Omega, 20 \Omega, j 10 \Omega, -j 20 \Omega$
- E) None of the above

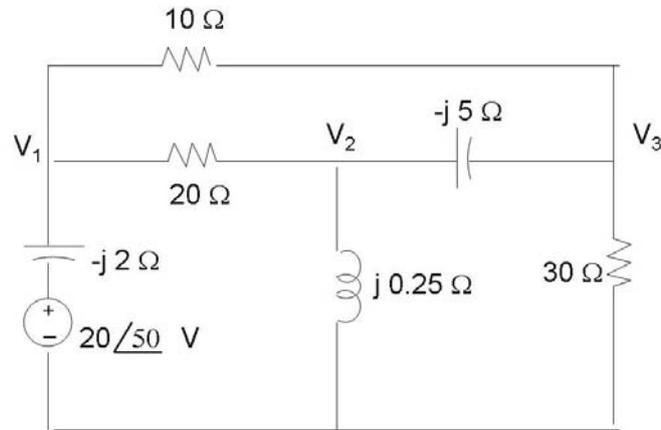**Problem 3**

Find the node equations for the following circuit



→ A)  $(0.15 + j0.5)V_1 - 0.05V_2 - 0.1V_3 + 7.66 - j6.43 = 0$   
 $-0.05V_1 + (0.05 - j3.8)V_2 - j0.2V_3 = 0$   
 $-0.1V_1 - j0.2V_2 + (0.133 + j0.2)V_3 = 0$

B)  $(0.15 + j0.5)V_1 - 0.1V_2 - 0.05V_3 + 7.66 - j6.43 = 0$   
 $-0.1V_1 + (0.1 - j3.8)V_2 - j0.2V_3 = 0$   
 $-0.05V_1 - j0.2V_2 + (0.0833 + j0.2)V_3 = 0$


C)  $(0.15 + j0.2)V_1 - 0.05V_2 - 0.1V_3 - 12.85 - j15.32 = 0$   
 $-0.05V_1 + (0.05 - j3.8)V_2 - j0.2V_3 = 0$   
 $-0.1V_1 - j0.2V_2 + (0.133 + j0.2)V_3 = 0$

D)  $(0.15 + j0.2)V_1 - 0.1V_2 - 0.05V_3 - 12.85 - j15.32 = 0$   
 $-0.1V_1 + (0.1 - j3.8)V_2 - j0.2V_3 = 0$   
 $-0.05V_1 - j0.2V_2 + (0.0833 + j0.2)V_3 = 0$

E) None of the above

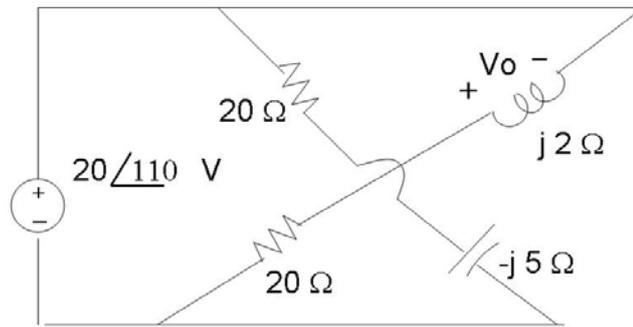
**Problem 4**

Find  $V_0(t)$  given  $\omega=120$  rad/sec.



- A)  $V_0 = -0.99 \cos(120t + 94.29^\circ)$  Volts
- B)  $V_0 = -1.99 \cos(120t + 194.29^\circ)$  Volts
- C)  $V_0 = -1.99 \cos(120t - 25.7^\circ)$  Volts
- D)  $V_0 = -0.99 \cos(120t - 115.71^\circ)$  Volts
- E) None of the above


**Problem 5**

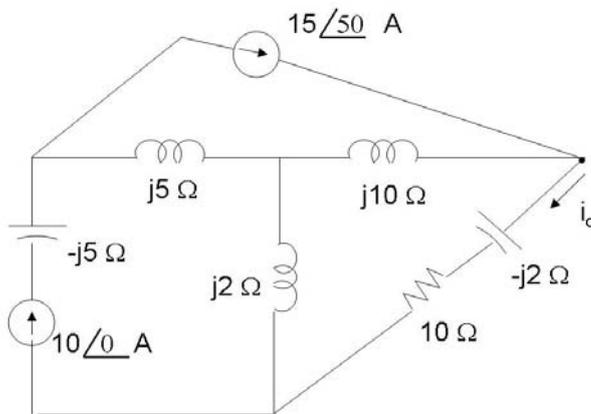

Find  $i_0$  in the circuit above.

- A)  $8.178 \angle 104.62^\circ$
- B)  $23.14 \angle 89.62^\circ$
- C)  $16.36 \angle 104.62^\circ$
- D)  $11.57 \angle 89.62^\circ$
- E) None of the above


**Problem 6**

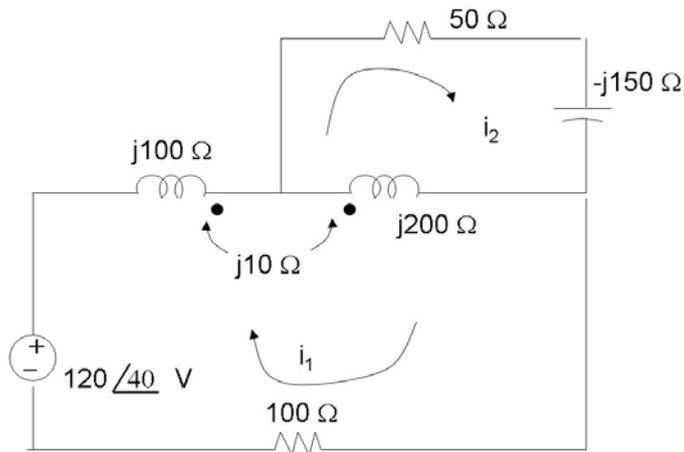

Given the circuit above, what are the two mesh equations?

- A)  $-120\angle 40^\circ + (100 + j280)i_1 - 190i_2 = 0;$        $-j190i_1 + (50 + j50)i_2 = 0$   
 B)  $-120\angle 40^\circ + (100 + j400)i_1 - 250i_2 = 0;$        $-j250i_1 + (50 + j50)i_2 = 0$   
 C)  $-120\angle 40^\circ + (100 + j200)i_1 - 150i_2 = 0;$        $-j150i_1 + (50 + j50)i_2 = 0$   
 D)  $-120\angle 40^\circ + (100 + j320)i_1 - 210i_2 = 0;$        $-j210i_1 + (50 + j50)i_2 = 0$   
 E) None of the above


**Problem 7**

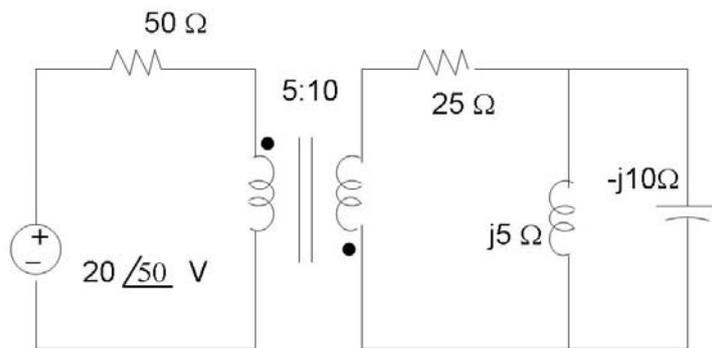

In the circuit shown above, what is the value of the reflected impedance of the 50 ohms resistor from the primary to the secondary side?

- A) 100 Ω  
 B) 12.5 Ω  
 C) 25 Ω  
 → D) 200 Ω  
 E) None of the above

### Problem 8

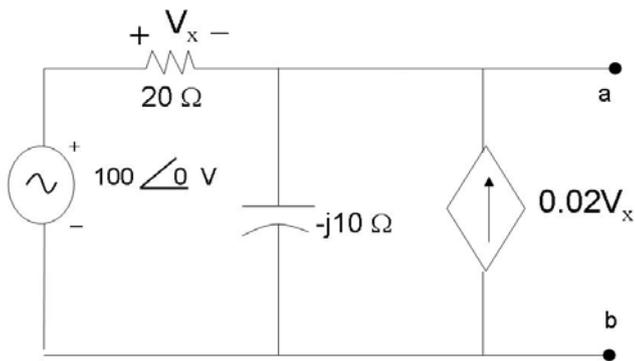

In the circuit shown above, find the Thevenin voltage across a,b


- A)  $76.82\angle -39.80^\circ \text{ V}$
- B)  $57.3\angle -55.0^\circ \text{ V}$
- C)  $28.6\angle -63.0^\circ \text{ V}$
- D)  $65.99\angle -48.3^\circ \text{ V}$
- E) None of the above

### Problem 9

For the same circuit of previous problem, find  $Z_{th}$  across a,b

- A)  $Z_{th} = 4.9 - j4.1 \Omega$
- B)  $Z_{th} = 1.08 - j2.12 \Omega$
- C)  $Z_{th} = 4.7 - j6.71 \Omega$
- D)  $Z_{th} = 3.7 - j5.1 \Omega$
- E) None of the above


**Problem 10**

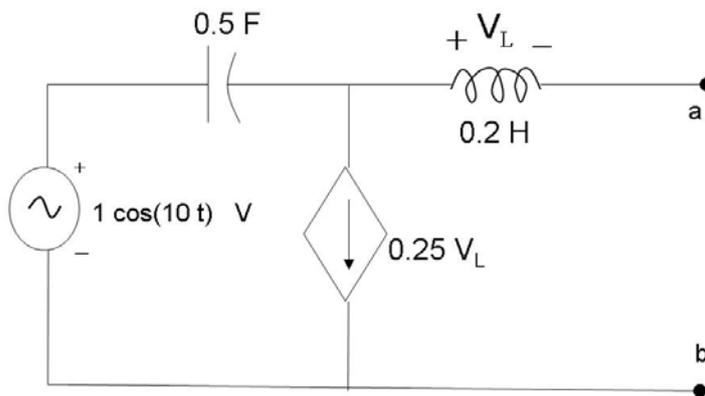

Find the Thevenin equivalent resistance and capacitance/inductance with respect to the terminals a,b in the circuit shown above

- A)  $R = 0.1\Omega$ ;  $L=0.18 \Omega$
- B)  $R = 0.2\Omega$ ;  $L=0.38 \Omega$
- C)  $R = 0.25\Omega$ ;  $L=0.43 \Omega$
- D)  $R = 0.15\Omega$ ;  $L=0.36 \Omega$
- E) None of the above


**Problem 11**

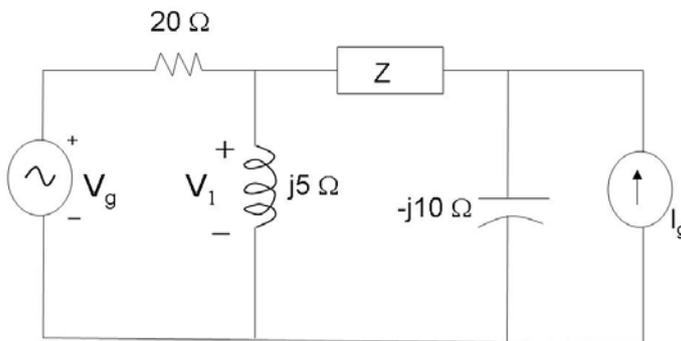

In the circuit shown above, find the value of the impedance  $Z$  if  $V_1 = 40 + j30 \text{ V}$ ,  $V_g = 100 - j50 \text{ V}$ , and  $I_g = 20 + j30 \text{ A}$

- A)  $10-j5 \Omega$
- B)  $58+j14 \Omega$
- C)  $68+j24 \Omega$
- D)  $5+j20 \Omega$
- E) None of the above

**Problem 12**

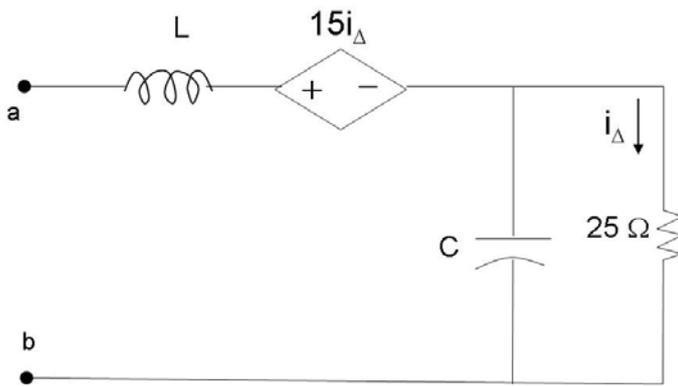

Find the input impedance  $Z_i$  at the terminals a,b in the circuit shown above


- A)  $Z_i = jL\omega + \frac{40}{1 + j25C\omega} \Omega$
- B)  $Z_i = jL\omega + \frac{25}{1 + j40C\omega} \Omega$
- C)  $Z_i = jL\omega + \frac{15}{1 + j40C\omega} \Omega$
- D)  $Z_i = jL\omega + \frac{40}{1 + j15C\omega} \Omega$
- E) None of the above

**Problem 13**

In the circuit of the previous problem, find the frequency  $\omega$  such that the input impedance  $Z_i$  is purely resistive.

- A)  $\omega = \frac{1}{40C} \sqrt{1000 \frac{C}{L} - 1} \text{ rad/s}$
- B)  $\omega = \frac{1}{25C} \sqrt{1000 \frac{C}{L} - 1} \text{ rad/s}$
- C)  $\omega = \frac{1}{40C} \sqrt{600 \frac{C}{L} - 1} \text{ rad/s}$
- D)  $\omega = \frac{1}{15C} \sqrt{600 \frac{C}{L} - 1} \text{ rad/s}$
- E) None of the above


**Problem 14**

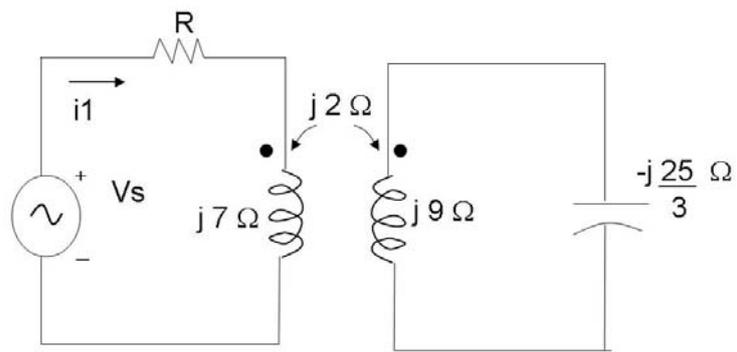

In the circuit shown above, it is given that  $R=1 \Omega$ , and  $V_s= 10\angle 0$  volts. Find the current  $i_1$  as indicated.

- A)  $8\angle -53.13^\circ$  A
- B)  $7.07\angle -53.13^\circ$  A
- C)  $7.07\angle -45^\circ$  A
- D)  $8\angle -45^\circ$  A
- E) None of the above


### Problem 5

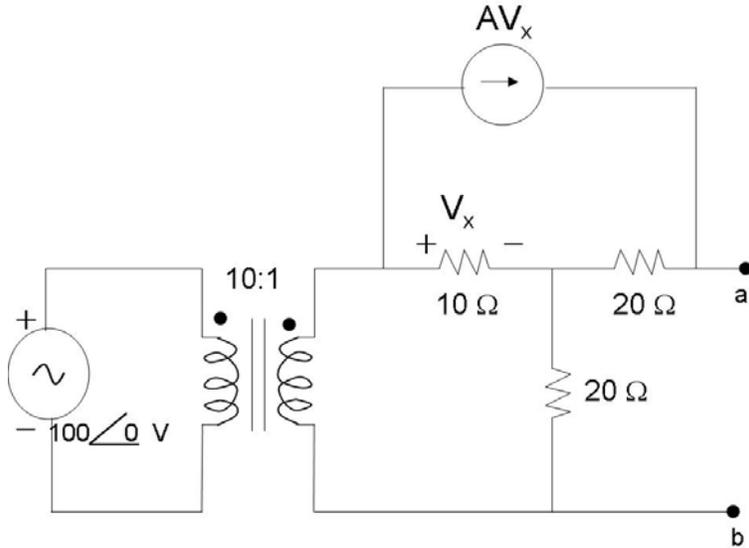

Find the magnitude of the Thevenin Voltage  $V_{th}$  across terminals a,b in the circuit above. Given  $A=1/4$ .

- A) 15.0 V
- B) 37.5 V
- C) 14.29 V
- D) 7.15 V
- E) None of the above


### Problem 7

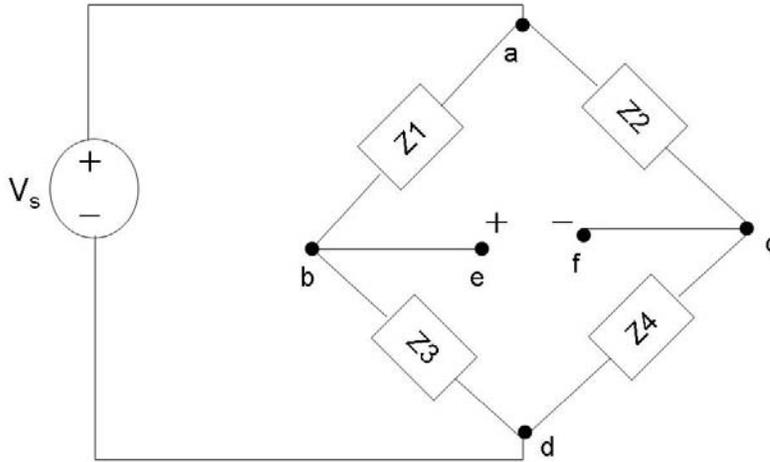

In the circuit shown above, given  $V_s = 48\angle 90^\circ$  V,  $Z_1 = 3 + j4 \Omega$ ,  $Z_2 = 8 - j6 \Omega$ ,  $Z_3 = 3 - j4 \Omega$  and  $Z_4 = 8 + j6 \Omega$ . The Thevenin equivalent circuit values for the voltage source and the internal impedance across terminals e and f are:

- A)  $14\angle 0^\circ$  V,  $3.5 - j3.5 \Omega$
- B)  $50\angle 0^\circ$  V,  $2.5 + j2.5 \Omega$ ,
- C)  $14\angle 0^\circ$  V,  $7.29 \Omega$
- D)  $50\angle 0^\circ$  V,  $10.42 \Omega$**
- E) None of the above


### Problem 8

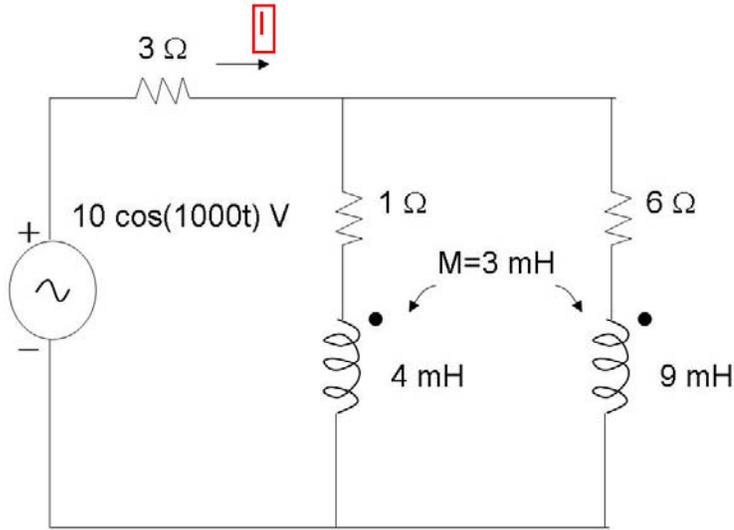

In the circuit shown above, the phasor form of the current  $I$  in amperes is:

- A)  $1.833 \angle -45.0^\circ \text{ V}$
- B)  $0.917 \angle -45.0^\circ \text{ V}$
- C)  $1.5 \angle -53.13^\circ \text{ V}$
- D)  $3.0 \angle -53.13^\circ \text{ V}$
- E) None of the above


**Problem 12**

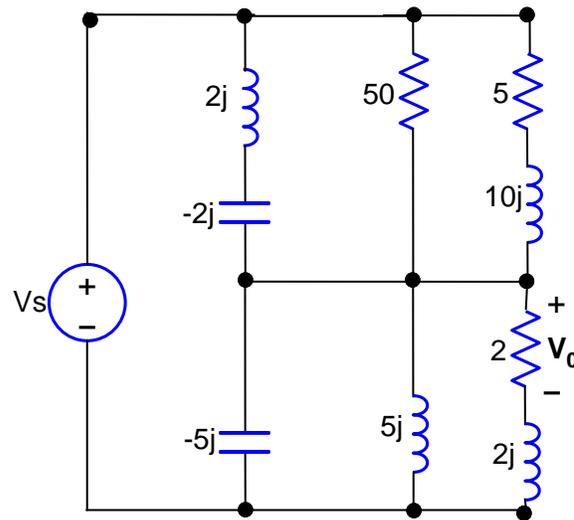

Find  $V_0$  if the source voltage is  $V_s = 20 \angle 60^\circ$  Volts.

- A)  $14.14 \angle 15^\circ$  V
- B)  $7.07 \angle 15^\circ$  V
- C)  $20 \angle 60^\circ$  V
- D)  $10 \angle 60^\circ$  V
- E) None of the above

**Problem 13**

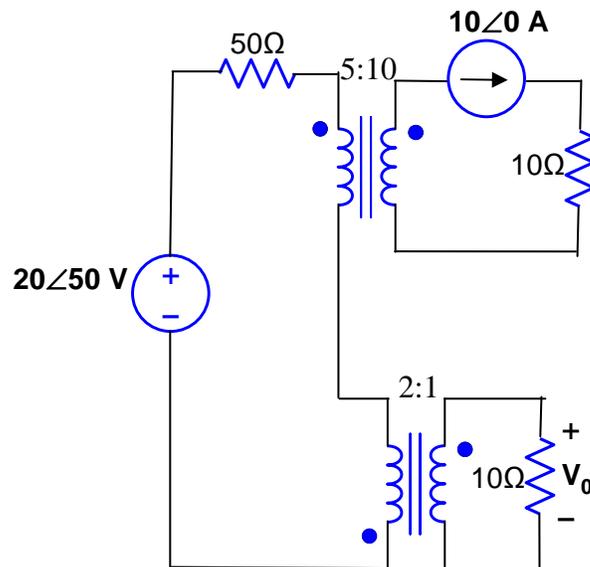


Find  $V_0$ .

- A)  $400 \angle 0^\circ$  V
- B)  $-400 \angle 0^\circ$  V
- C)  $100 \angle 0^\circ$  V
- D)  $-100 \angle 0^\circ$  V
- E) None of the above


3. Determine the Thevenin impedance to the left of the terminals T1-T2 of the circuit shown in figure.

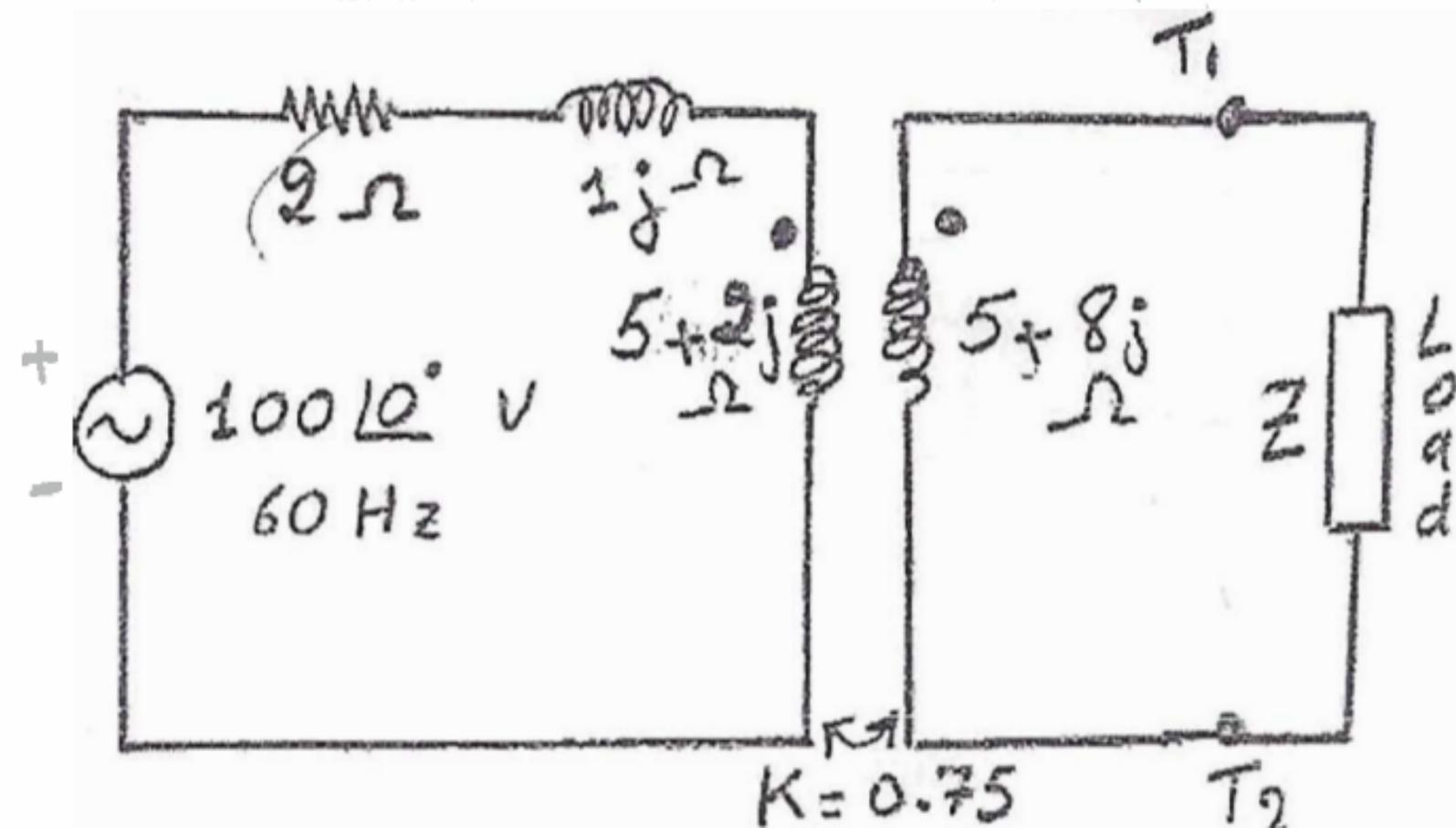- a.  $15 \angle 50^\circ \Omega$
- b.  $5 + 5j \Omega$
- c.  $1.086 + 2.535j \Omega$
- d.  $9.69 \angle 51.07^\circ \Omega$
- e. None of the above.




5. Find the voltage  $v_o(t)$  across the capacitor of the circuit shown in figure.

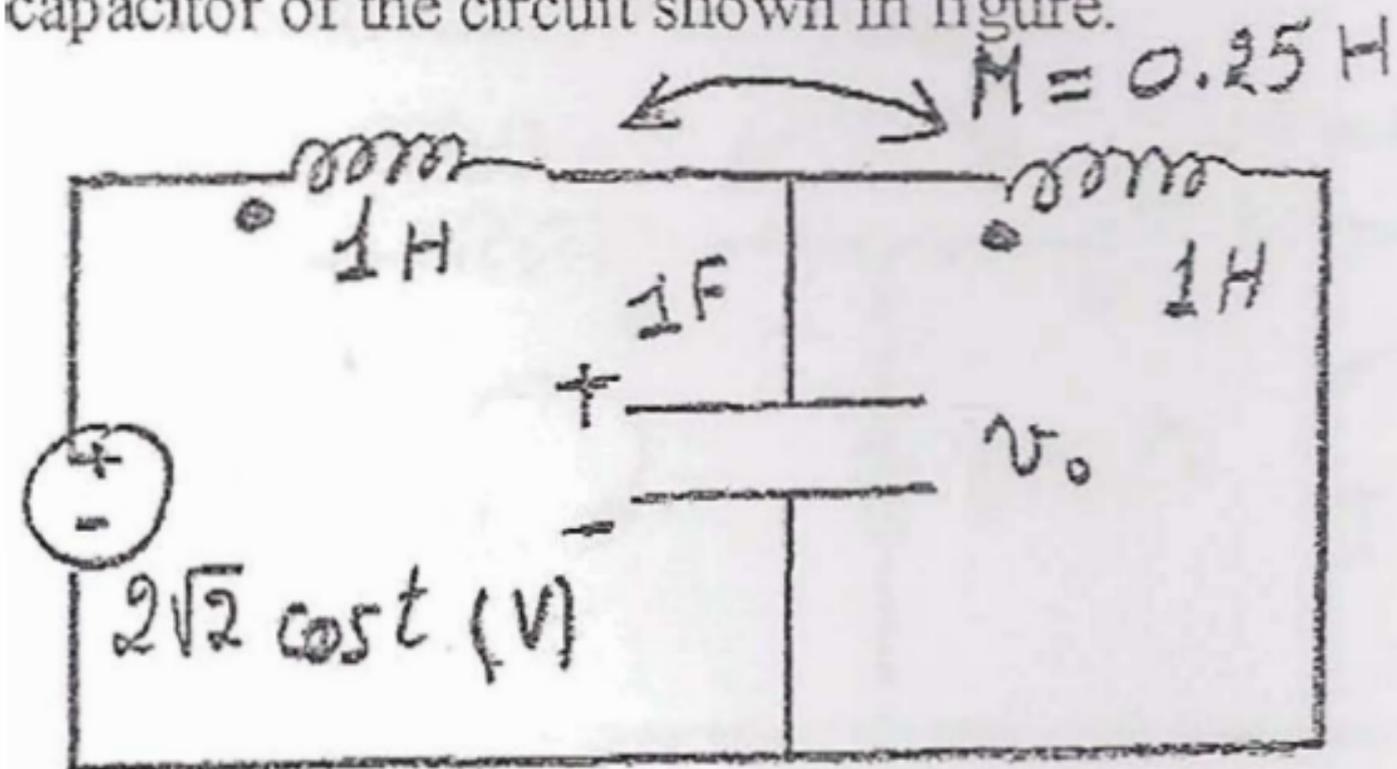- a.  $1.60 \cos(2t)$  V.
- b.  $1.60 \sin(t)$  V.
- c.  $3.2 \cos(t)$  V.
- d.  $2.26 \cos(t)$  V.
- e. None of the above.



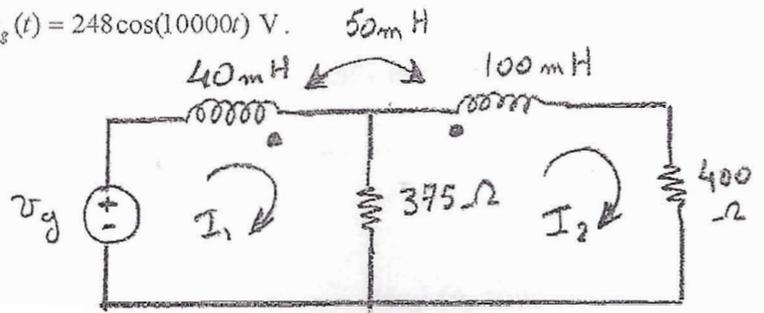9. Find  $I_1$  in the figure shown if  $v_g(t) = 248\cos(10000t)$  V.




- a.  $0.8 - 0.62j$  A
- b.  $0.4 - 0.3j$  A
- c.  $0.6 - 0.6j$  A
- d.  $0.9 - 0.31j$  A
- e. None of the above.

10. In problem 9, find the average power delivered to the  $375 \Omega$  resistor.

- a. 99.2 W.
- b. 50.3 W.
- c. 49.2 W.
- d. 62.7 W.
- e. None of the above.

11. Calculate the reading of the two wattmeters ( $W_1 + W_2$ ) in the circuit shown in figure. The value of  $Z_\phi = 60\angle 30^\circ \Omega$ .

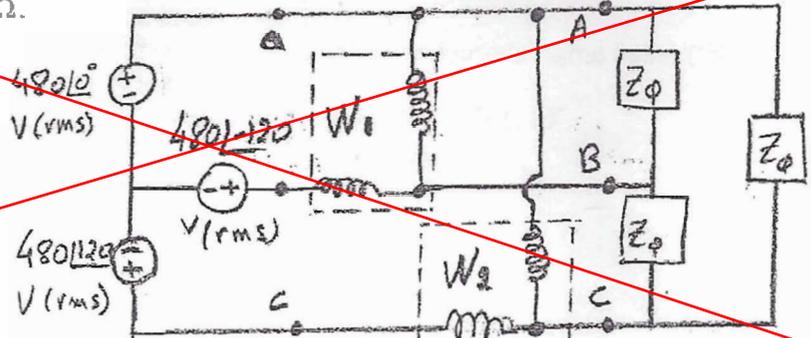
- a. ~10 kW.
- b. ~29.9 kW.
- c. ~33.2 kW.
- d. ~15.4 kW.
- e. None of the above.



12. Find the steady-state expression for  $v_o(t)$  in the circuit shown if  $v_{g1}(t) = 10\cos(5000t + 53.13^\circ)$  V and  $v_{g2}(t) = 8\sin(5000t)$  V.


- a.  $4\cos(5000t)$  V.
- b.  $8\cos(5000t)$  V.
- c.  $16\cos(5000t)$  V.
- d.  $12\cos(5000t)$  V.
- e. None of the above.

$22.3\cos(5,000t + 29.7)$

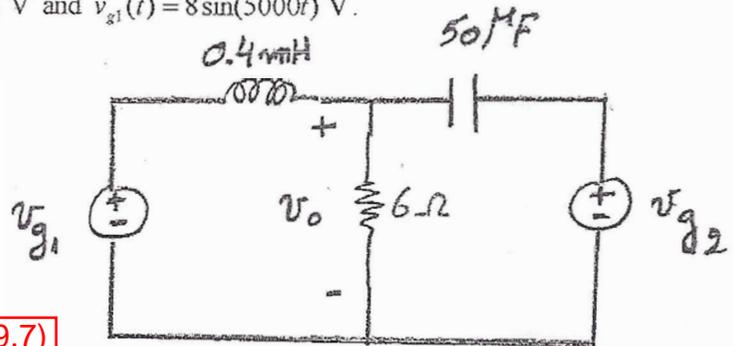

**Problem 8 ( 14 pts)**

Consider the circuit shown

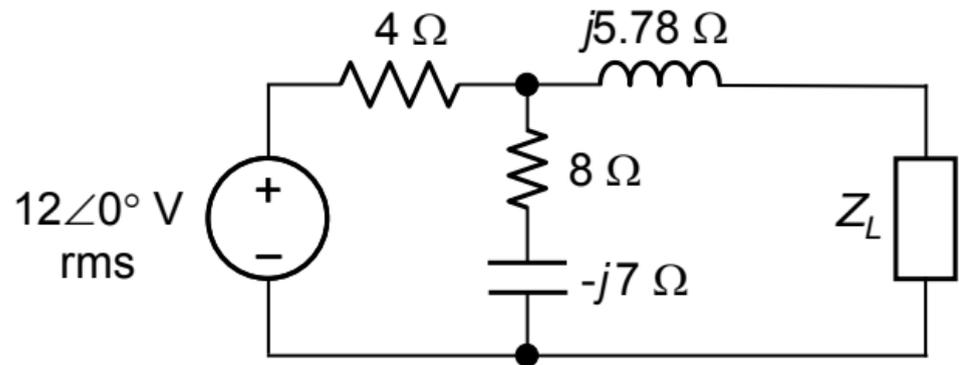

- a. For  $Z_L = 3 - j5.2 \Omega$ , determine the average power developed by the voltage source and the average power absorbed by the load. (4 pts)

$$\mathbf{V}_{Th} = 12 \frac{8 - j7}{12 - j7} = 9 - j1.74 \text{ V};$$


$$|\mathbf{V}_{Th}| = 9.18 \text{ V};$$

$$\mathbf{I}_L = \mathbf{V}_{Th} / 6 = 1.5 - j0.29 \text{ A}; \quad 12 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_1 = (3 - j0.58) \mathbf{I}_L = 4.68 + j0 \text{ V rms}$$

$$\mathbf{I}_{SRC} = \frac{12 - 4.68}{4} = 1.83 + j0 \text{ A}$$

$$P_{SRC} = V_1 I_{SRC} = 12 \times 1.83 \cong 22 \text{ W}; \quad P_L = \frac{(9.18)^2}{4 \times 3} \cong 7 \text{ W}.$$

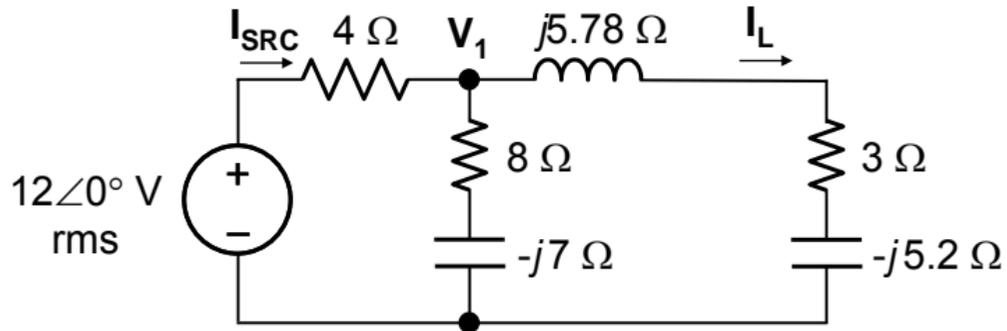

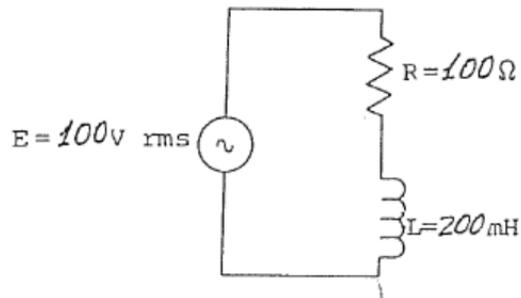


Figure 3.

3. Determine the power dissipated in the load in the circuit shown in figure 3.  
 $f = 60\text{ Hz}$ .
- A. 38.8 W
  - B. 63.8 W
  - C. 52.5 W
  - D. 45.3 W
  - E. None of the above


1. A coil (R and L) has a resistance of  $10\Omega$  and draws a current of 5A (RMS) when connected across a 100V (RMS), 60 Hz source. Determine the inductance of the coil.

- a. 17.32 mH
- b. 32.48 mH
- c. 45.94 mH
- d. 102.73 mH
- e. None of the above

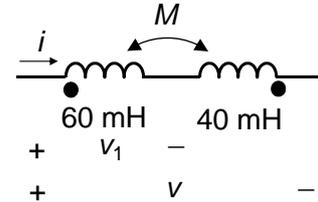1. If  $M = 5 \text{ mH}$ , determine the ratio  $v_1/v$ .


**Solution:**  $L_{eq} = L_1 + L_2 - 2M$ ;  $v = L_{eq} \frac{di}{dt}$ ;  $v_1 = L_1 \frac{di}{dt} - M \frac{di}{dt}$ ;

hence, 
$$\frac{v_1}{v} = \frac{L_1 - M}{L_1 + L_2 - 2M} = \frac{60 - M}{100 - 2M}$$



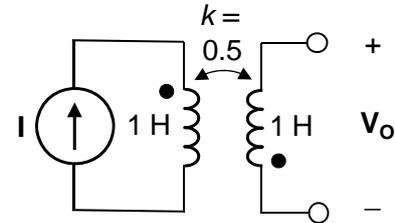
2. Determine  $\mathbf{V}_o$ , given that  $\mathbf{I} = 1 \angle 0^\circ \text{ A}$  and  $\omega = 10 \text{ rad/s}$ .

**Solution:**  $M = k\sqrt{L_1 L_2} = 0.5 \text{ H}$ ; secondary voltage is  $j\omega M$ , with the dotted terminal positive with respect to the undotted terminal. Hence,  $\mathbf{V}_o = -j\omega M \mathbf{I} = -j10 \times 0.5 \mathbf{I} = -j5 \mathbf{I}$ .



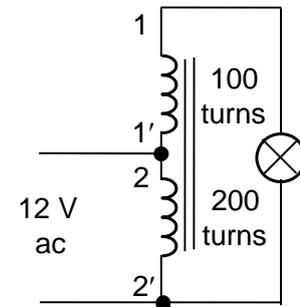3. The lamp glows brighter when the dots are at coil terminals

**Solution:** The lamp glows brighter when the voltage across it is largest. This occurs when the voltages across the windings are additive, that is, when the dots are at terminals 1 and 2 or 1' and 2'.



6. Derive the time-domain expression for  $v_C$ ,  
given that  $v_{SRC} = 10\sin(2,000t)$  V.

**Solution:**  $\omega L = 2 \times 10^3 \times 2 \times 10^{-3} = 4 \Omega$ ;

$$\frac{1}{\omega C} = \frac{1}{2 \times 10^3 \times 100 \times 10^{-6}} = 5 \Omega; \mathbf{V}_{SRC} = 10 \angle 0^\circ.$$

The node-voltage method can be applied,  
the circuit being as shown. At the middle node:



$$\mathbf{V}_C / -j5 + (\mathbf{V}_C - \mathbf{V}_x) / j4 + (\mathbf{V}_C - 10) / j4 = 0$$

At the right-hand node:

$$(\mathbf{V}_x - \mathbf{V}_C) / j4 + (\mathbf{V}_x - 10) / 3 = 5\mathbf{I}_x = 5(10 - \mathbf{V}_C) / j4$$

Solving,  $\mathbf{V}_C = 11.98 + j1.44 = 12.1 \angle 6.86^\circ$ , so that
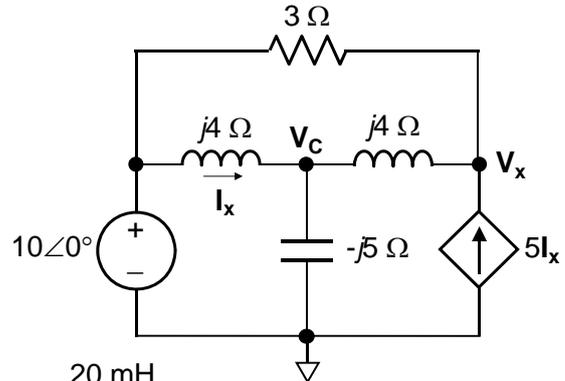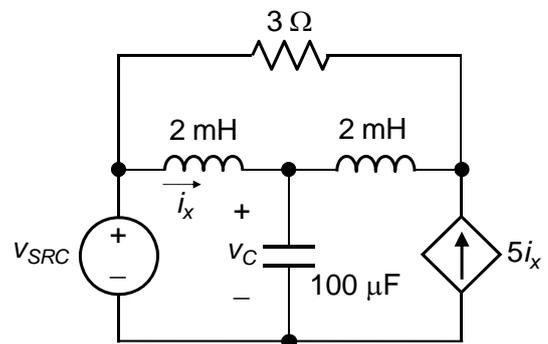
$$v_C = 12.1 \sin(2,000t + 6.86^\circ) \text{ V}.$$



7. Derive  $\mathbf{V}_{Th}$  and  $Z_{Th}$  as  
seen between terminals  
ab, given that  $v_{SRC} =$   
 $10\cos(1,000t + 45^\circ)$  V.

**Solution:**  $\omega L_1 =$

$$10^3 \times 30 \times 10^{-3} = 30 \Omega; \omega L_2$$

$$= \omega M = 10^3 \times 20 \times 10^{-3} = 20$$

$$\Omega; \frac{1}{\omega C} = \frac{1}{10^3 \times 50 \times 10^{-6}}$$



$$= 20 \Omega; \mathbf{V}_{SRC} = 10 \angle 45^\circ.$$

The circuit in the

frequency domain will be as shown, where  $\omega(L_1 - M) = 10 \Omega$ ;  $\omega(L_2 - M) = 0 \Omega$  and is omitted.

The  $j20 \Omega$  in parallel with  $-j20 \Omega$  is effectively an open circuit. The current in the  $(5 + j10) \Omega$

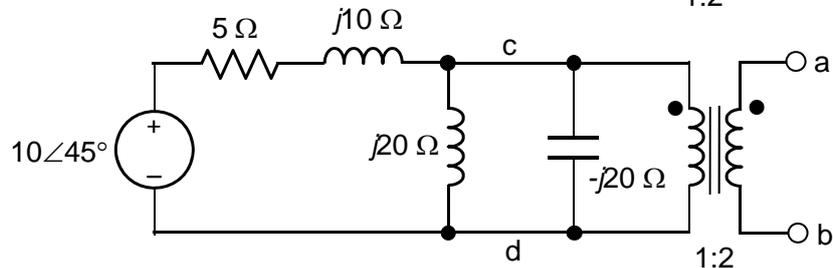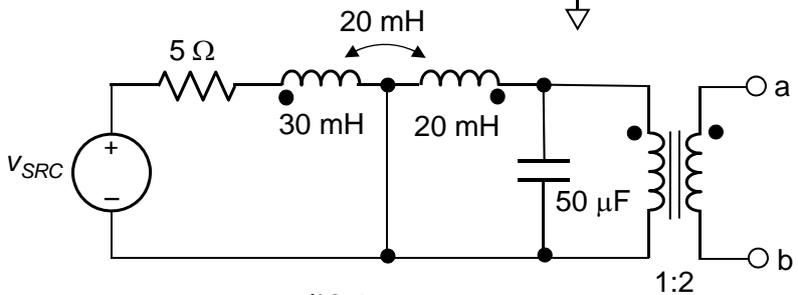impedance is zero,  $\mathbf{V}_{cd} = 10 \angle 45^\circ$ , and  $\mathbf{V}_{ab} = \mathbf{V}_{Th} = 20 \angle 45^\circ$ .




If the independent voltage source is replaced by a short circuit, the impedance on the primary side is  $(5 + j10) \Omega$  and  $Z_{Th} = 4(5 + j10) = 20 + j40 \Omega$ .

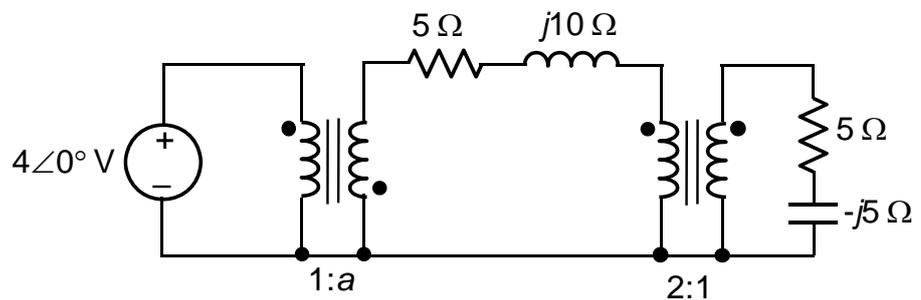3. Determine the impedance seen by the source, assuming  $a = 2$ .

**Solution:** Reflection of the  $(5 - j5) \Omega$


through the RH transformer gives  $(20 - j20) \Omega$ . The impedance on the secondary side of the LH transformer is  $(25 - j10) \Omega$ . Reflected to the primary side, this becomes  $(25 - j10)/a^2 \Omega$ .



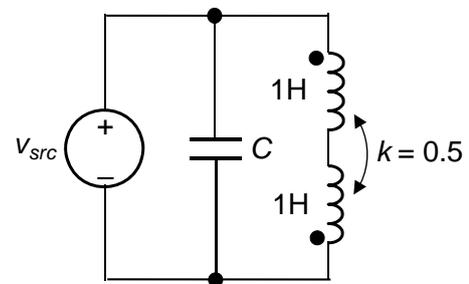4. If  $v_{src} = 10\cos(1,000t) \text{ V}$ , determine the energy stored in the circuit in the sinusoidal steady state at  $t = 0$ , assuming  $C = 1 \mu\text{F}$ .

**Solution:** At  $t = 0$ , the voltage across  $C$  is 10 V and the current through the inductors is zero, being proportional to the integral of  $v_{src}$ . The energy stored

is  $W = \frac{1}{2} C v^2 = 50 \text{ C}$ .




5. Determine  $R_x$  given that  $\mathbf{I} = 0$  and  $R = 2 \Omega$ .

**Solution:** Since  $\mathbf{I} = 0$ , the voltage across  $R_x$  is 10 V, and the same current  $\frac{30\angle 0^\circ - 10\angle 0^\circ}{R}$  flows


through  $R$  and  $R_x$ . It follows that
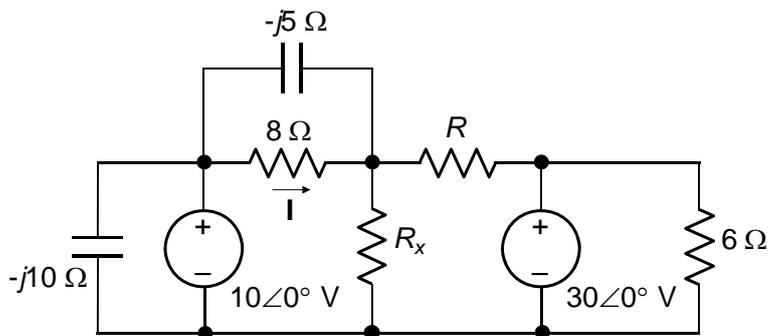
$$\frac{20}{R} R_x = 10, \text{ or } R_x = \frac{R}{2}.$$



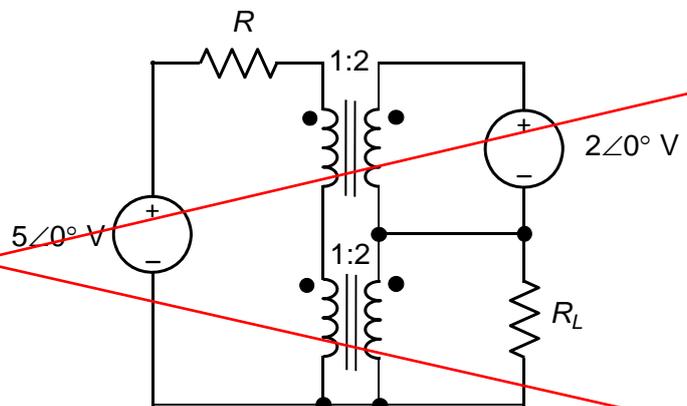7. Determine the maximum power that can be delivered to  $R_L$ , assuming  $R = 0.5 \Omega$ .

**Solution:** The primary voltage of the upper transformer is always 1 V. On



9. Two identical coils, each having an inductance of 10 mH, are connected in series. When the connections to one of the coils are reversed, the total inductance is multiplied by a factor  $a$ . Determine the coupling coefficient of the coils.

**Solution:**  $(10 + 10 + 2M) = a(10 + 10 - 2M)$ ;  $2M(a + 1) = 20(a - 1)$ ;

$$M = \frac{10(a-1)}{a+1}; \quad k = \frac{M}{10} = \frac{(a-1)}{a+1}$$

10. Determine  $I_x$ , assuming  $R = 4 \Omega$ .


**Solution:** The voltage across all windings is zero. Hence,  $I_1 = \frac{10}{R}$  A, and

$$I_2 = \frac{4}{2} = 2 \text{ A. Setting the net mmf to}$$

zero,  $400I_1 - 100I_2 + 200I_3 = 0$ , or

$$\frac{4 \times 10}{R} - 2 + 2I_3 = 0, \text{ which gives } I_3 =$$
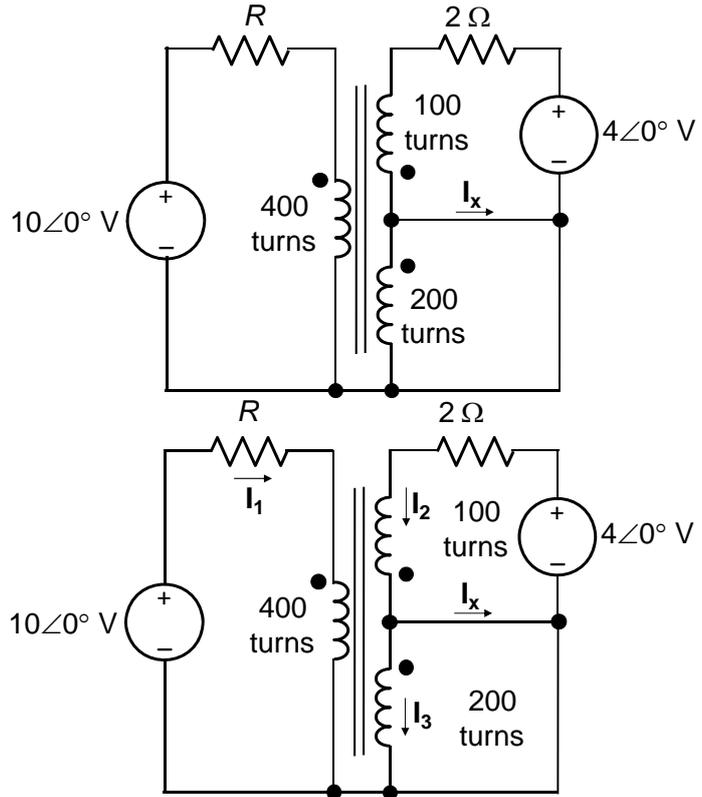
$$1 - \frac{20}{R}; \quad I_x = I_2 - I_3 = 1 + \frac{20}{R}.$$




11. Determine the frequency at which maximum power is dissipated in the  $10\ \Omega$  resistor, assuming  $L = 1\ \text{H}$ .

**Solution:**  $\frac{1}{\omega C} = \frac{1}{\omega}\ \Omega$ . Maximum power is

dissipated in the  $10\ \Omega$  resistor when  $X_L = -X_C$ ,

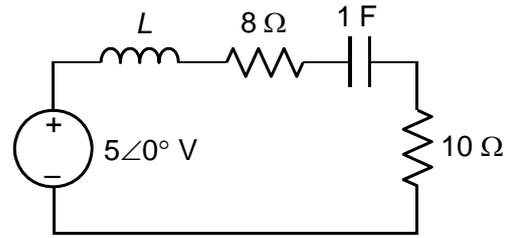which gives  $\omega L = \frac{1}{\omega}$ , or  $\omega = \frac{1}{\sqrt{L}}$  rad/s.



15. Determine the total power dissipated in  $R$  if  $R = 1\ \Omega$ .

**Solution:** With either of the  $10\cos 100t\ \text{V}$  acting alone,  $i_{R1} =$

$$\frac{10}{2 + \frac{2R}{R+2}} \times \frac{2}{R+2} = \frac{5}{R+1}$$


The current due to both  $10\cos 100t\ \text{V}$  sources, with the  $10\cos 200t\ \text{V}$

source set to zero, is  $\frac{10}{R+1}$  and the power dissipated in  $R$  is  $\frac{100R}{2(R+1)^2} = \frac{50R}{(R+1)^2}$ . With the

$10\cos 200t\ \text{V}$  source acting alone,  $i_{R3} = \frac{10}{R+1}$ , and the power dissipated in  $R$  is


$$\frac{100R}{2(R+1)^2} = \frac{50R}{(R+1)^2}$$

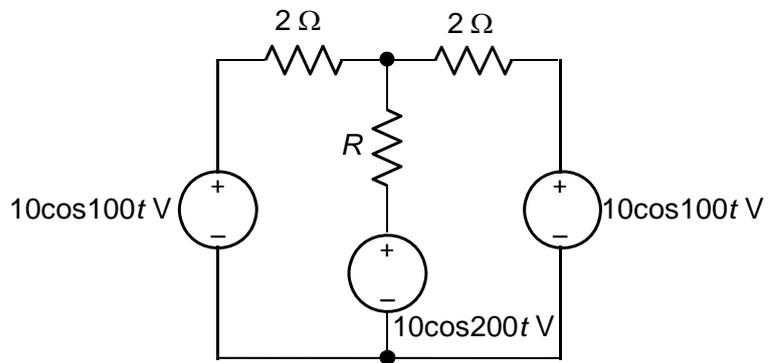The total power dissipated in  $R$  is  $\frac{100R}{(R+1)^2}$ .



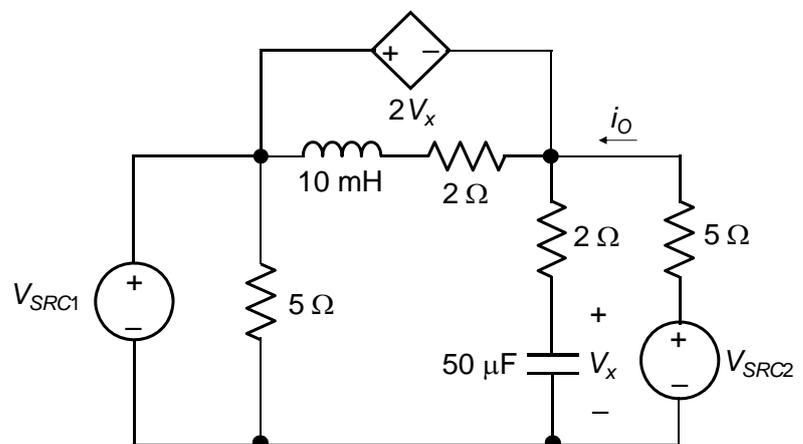
16. Determine  $i_o$ , given that

$V_{SRC1}$  is  $15\ \text{V}$  dc and  $V_{SRC2} = 10\cos(3,000t)\ \text{V}$ .




**Solution:** With  $V_{SRC1}$  applied and  $V_{SRC2}$  set to zero, the circuit becomes as shown.  $15 = 3V_x$ , so that  $V_x = 5$  V and  $I_{O1} = \frac{-V_x}{5} = -1$

A.

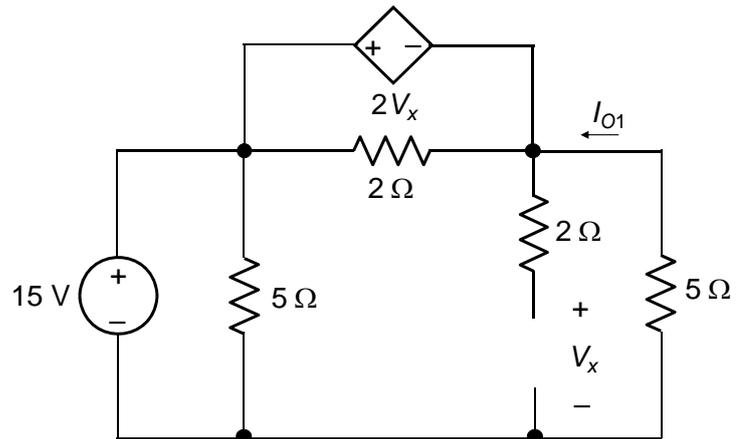

With  $V_{SRC2}$  applied and  $V_{SRC1}$  set to zero, the circuit becomes as shown. It follows that:  $-2V_x = V_x + \frac{2V_x}{jX_C}$ , or  $V_x \left( 3 + \frac{2}{jX_C} \right) = 0$ , which

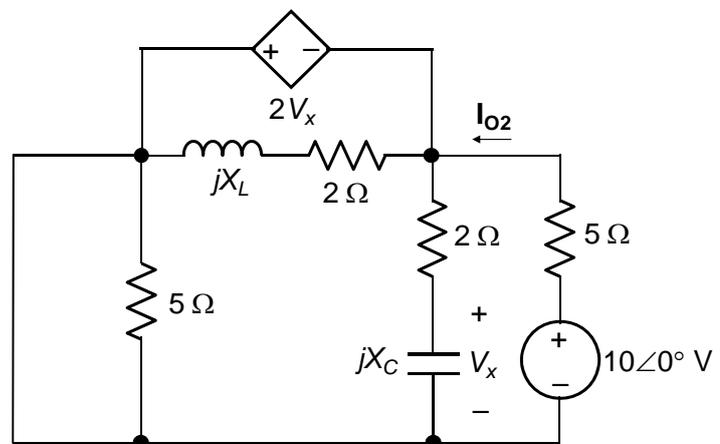gives  $V_x = 0$ . Hence,  $I_{O2} = \frac{10\angle 0^\circ}{5} = 2\angle 0^\circ$  A. Thus,  $i_O = -1 + 2\cos(3,000t)$  A.




17. Determine  $k$  so that the input resistance is purely resistive.

**Solution:** Disregarding the  $10 \Omega$  resistance and replacing the linear transformer by its T-equivalent circuit, the circuit becomes as shown. The input reactance is

$$j10 + jX_M - \frac{jX_M(j20 + jX_M)}{j20} = 0, \text{ or}$$

$$10 + X_M - X_M - \frac{X_M^2}{20} = 0, \text{ which gives}$$
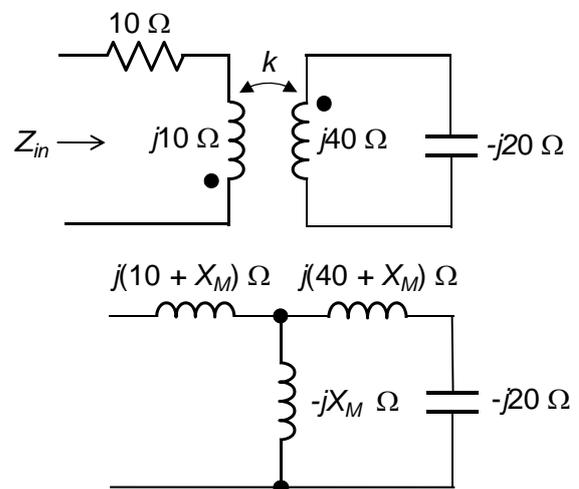
$$X_M = \sqrt{200} = 10\sqrt{2}. \text{ Hence, } k = \frac{10\sqrt{2}}{\sqrt{400}} = \frac{1}{\sqrt{2}} = 0.71.$$




## Problem 1

Given 3 elements  $R = 10K\Omega$ ,  $L = 10mH$  and  $C = 625nF$  powered by a source  $v = 90\sin(10,000t + \frac{\pi}{4})$  (V). Find the impedance of each element  $Z_R$ ,  $Z_L$  and  $Z_C$ .

- A)  $Z_R = 10K\Omega$ ,  $Z_L = 100j\Omega$ ,  $Z_C = -160j\Omega$   
B)  $Z_R = 10K\Omega$ ,  $Z_L = 10j\Omega$ ,  $Z_C = -16j\Omega$   
C)  $Z_R = 10jK\Omega$ ,  $Z_L = 10j\Omega$ ,  $Z_C = -1600j\Omega$   
D)  $Z_R = 10K\Omega$ ,  $Z_L = 10j\Omega$ ,  $Z_C = -160j\Omega$   
E) None of the above
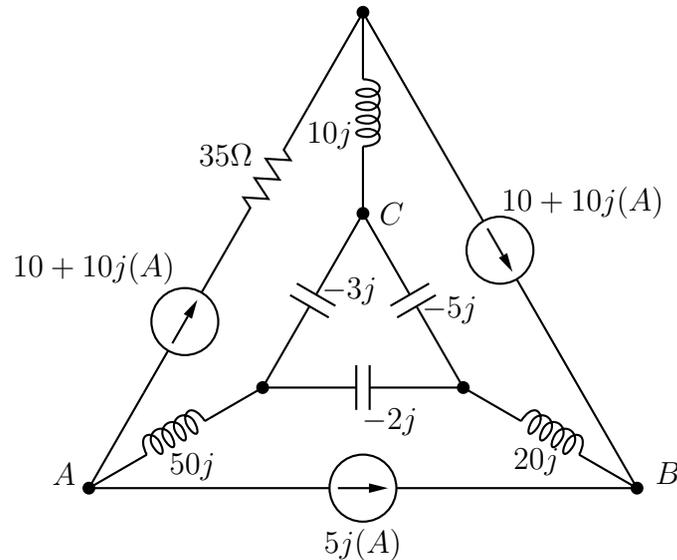
## Problem 2


Find the Thevenin equivalent voltage between A and C. (Impedances are in  $\Omega$ )



- A) 285-190j V  
→ B) -741+494j V  
C) -741-494j V  
D) 285+190j V  
E) None of the above
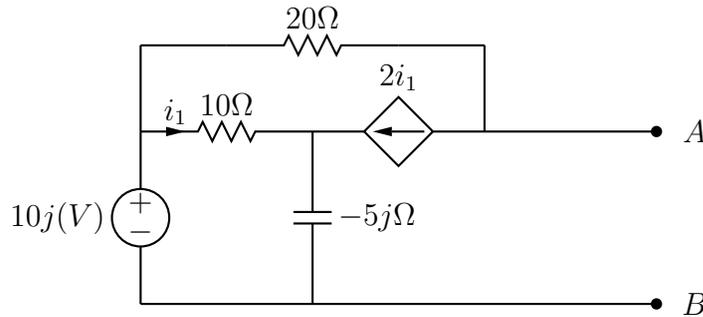
### Problem 3


Find the Thevenin equivalent voltage between A and B.



- A)  $39.7V \angle 21.6^\circ$
- B)  $18.6V \angle 7.1^\circ$
- C)  $18.6V \angle -7.1^\circ$
- D)  $39.7V \angle -21.6^\circ$
- E) None of the above
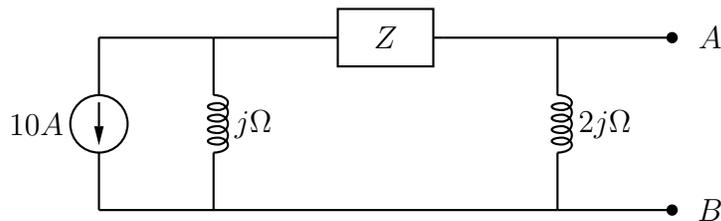
### Problem 4


Find the nature of Z such that the Thevenin equivalent impedance between A and B is  $1\Omega$ .



- A)  $0.8 - 1.4j\Omega$
- B)  $0.8 + 1.4j\Omega$
- C)  $0.5 - 2.5j\Omega$
- D)  $0.5 + 2.5j\Omega$
- E) None of the above
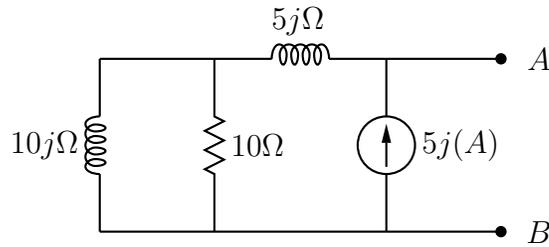
### Problem 5

Find the Thevenin voltage between A and B.



A)  $50+25j$  V

B)  $-100+50j$  V


C)  $100+50j$  V

→ D)  $-50+25j$  V

E) None of the above
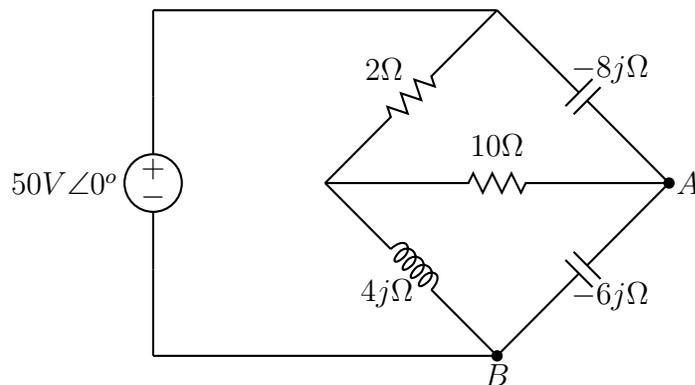
### Problem 6

Find the Thevenin impedance between A and B.



A)  $1.49-0.55j$   $\Omega$

→ B)  $0.96+3.21j$   $\Omega$


C)  $0.96-3.21j$   $\Omega$

D)  $1.49+0.55j$   $\Omega$

E) None of the above
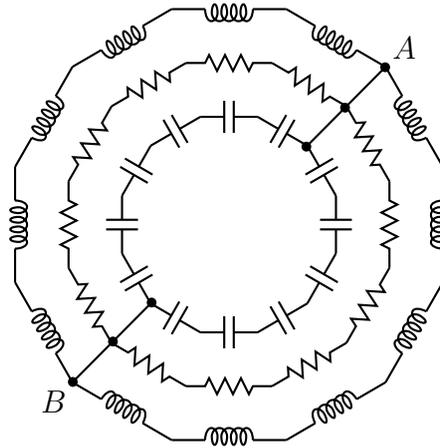
## Problem 7


All the inductors are equal to  $5j\Omega$ , all the capacitors are equal to  $-6j\Omega$ , all the resistances are equal to  $10\Omega$ . Find  $Z_{AB}$ .



- A)  $30.56+16.98j \Omega$
- B)  $30.56-16.98j \Omega$
- C)  $27-9j \Omega$
- D)  $27+9j \Omega$
- E) None of the above

## Problem 8


Find  $i_1$ .

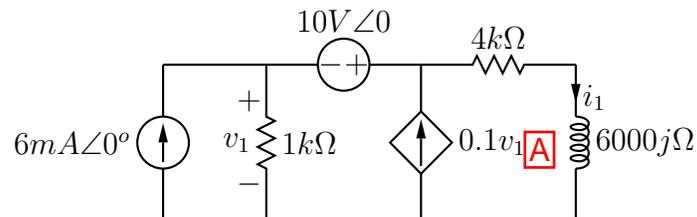

- A)  $0.76-1.14j \text{ mA}$
- B)  $-0.26+1.6j \text{ mA}$
- C)  $0.26-1.6j \text{ mA}$
- D)  $-0.76+1.14j \text{ mA}$
- E) None of the above

## Problem 9


Find  $i_1$ .

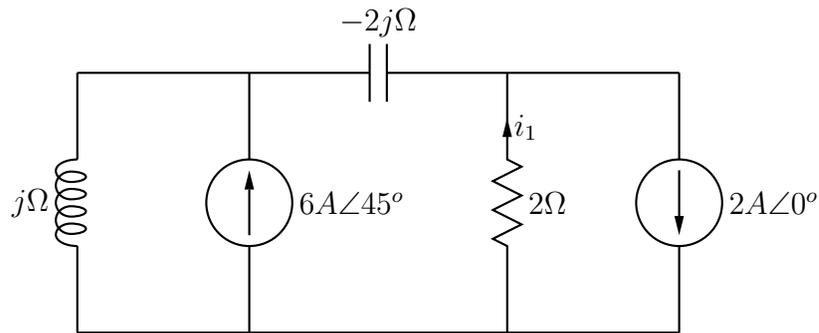

- A)  $3.38\angle -29.2^\circ$  (A)
- B)  $7.55\angle -82.4^\circ$  (A)
- C)  $7.55\angle 82.4^\circ$  (A)
- D)  $3.38\angle 29.2^\circ$  (A)
- E) None of the above
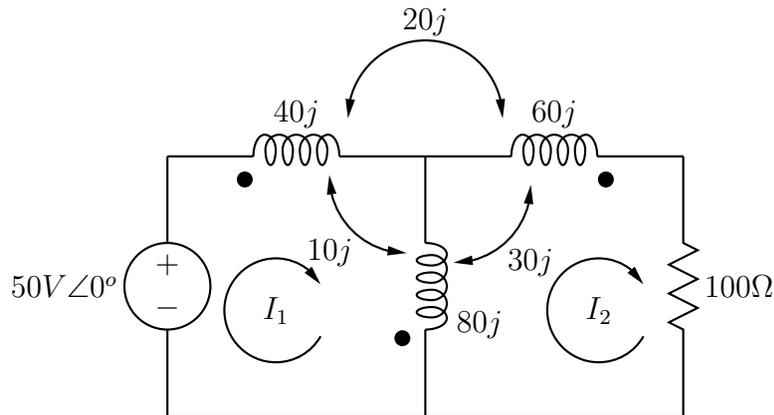
## Problem 10


Write the two mesh current equation for  $I_1$  and  $I_2$  **Don't solve**. (Impedances are in  $\Omega$ ).



- A)  $100jI_1 + 60jI_2 = 50$        $60jI_1 + (100 + 80j)I_2 = 0$
- B)  $120jI_1 - 80jI_2 = 50$        $-80jI_1 + (100 + 80j)I_2 = 0$
- C)  $100jI_1 - 80jI_2 = 50$        $-80jI_1 + (100 + 80j)I_2 = 0$
- D)  $100jI_1 - 60jI_2 = 50$        $-60jI_1 + (100 + 80j)I_2 = 0$
- E) None of the above
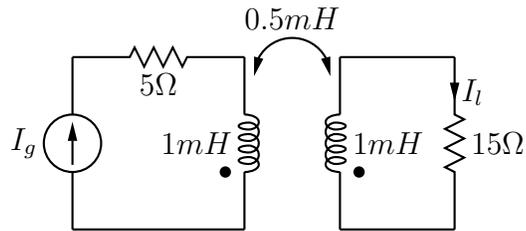
## Problem 11


If  $I_g = 20\cos(10,000t + \frac{\pi}{3})(A)$  find the energy associated with the 2 coils at the time  $t = 100\pi\mu s$ .



- A) 65.3mJ
- B) 261.3mJ
- C) 40.7mJ
- D) 163mJ
- E) None of the above
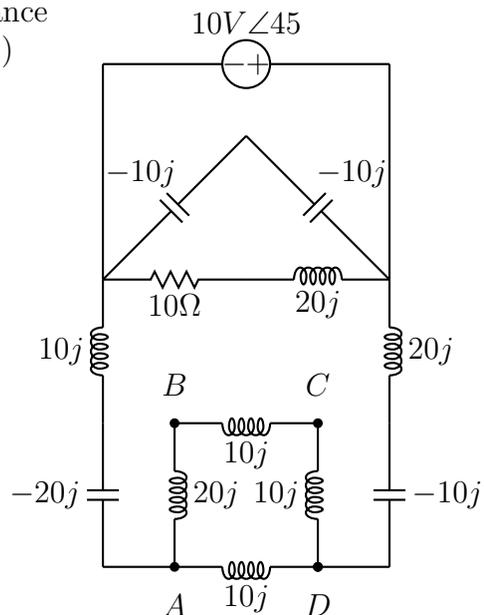
## Problem 12


Find the Thevenin equivalent impedance between A and B. (Impedances are in  $\Omega$ .)



- A)  $10j \Omega$
- B)  $8j \Omega$
- C)  $7.5j \Omega$
- D)  $12j \Omega$
- E) None of the above
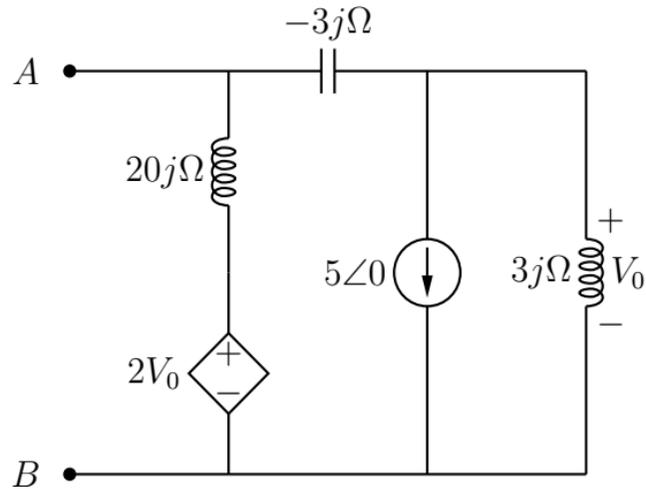
## Problem 1


Find the Thevenin equivalent voltage between A and B ( $V_{AB}$ ).



- A)  $15j$  V
- B)  $-20j$  V
- C)  $20j$  V
- D)  $-15j$  V
- E) None of the above
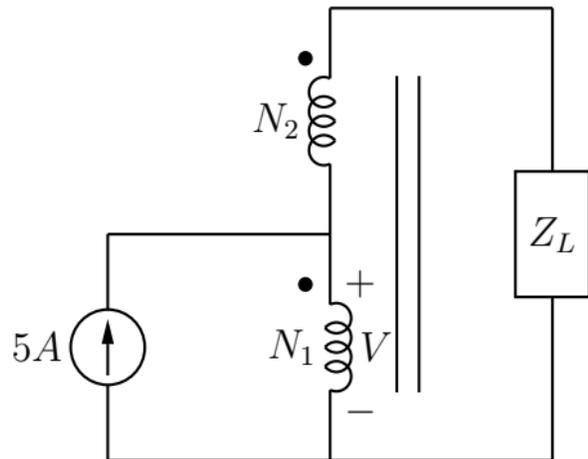
## Problem 9


Given  $Z_L = 100 + 100j$ ,  $N_2=90$ ,  $N_1=10$ , find  $V$ .



- A)  $7.07V \angle -135^\circ$
- B)  $63.64V \angle 45^\circ$
- C)  $63.64V \angle -135^\circ$
- D)  $7.07V \angle 45^\circ$
- E) None of the above
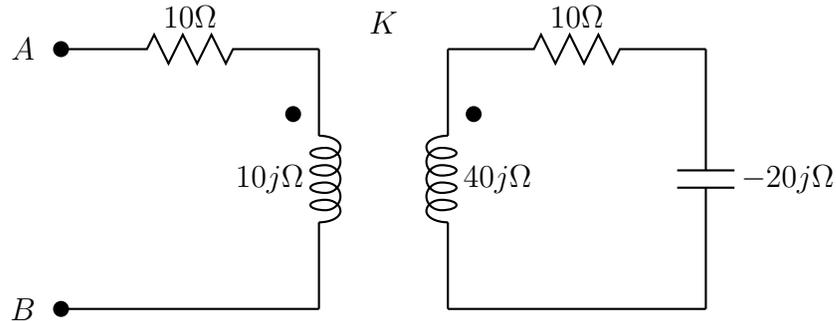
## Problem 16


Consider the linear transformer of the figure below, given  $\omega = 1 \text{ rad/s}$ , find the coupling coefficient  $K$ , such that the Thevenin impedance between A and B is purely resistive.



- A) 0.79
- B) 0.82
- C) 0.85
- D) 0.88
- E) None of the above

## Problem 17

Find  $I$ .

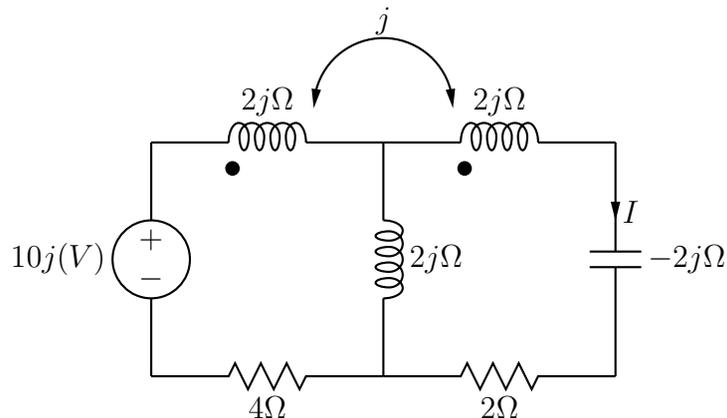

- A)  $0.0389 - 0.6226j$  A
- B)  $-0.0778 + 1.2452j$  A
- C)  $-0.0389 + 0.6226j$  A
- D)  $0.0778 - 1.2452j$  A
- E) None of the above